

<b>Student Name</b>
Nayan Raj Khanal

<b>Student Number</b>
2227486

# **Portfolio Introduction**

**Workshop Activities 50% Weighting**

**Mini Project 50% Weighting**

**This completed portfolio will need submitting to Canvas by the due date.**

**Questions please email**

**Dr Sarah Slater**

**s.i.slater@wlv.ac.uk**

# Portfolio

## Contents

Workbook 1	4
Activity 1.1: Actual voltage across 5V breadboard pins.	4
Activity 1.2: Actual voltage across 3.3V breadboard pins.	4
Activity 1.3: Potential Divider Calculations	4
Activity 1.4: 3V Calculations from either the 5V supply or 3.3V supply	5
Activity 1.5: Voltage Divider circuit readings from Breadboard circuit.	6
Activity 1.6: LED Circuits	6
Activity 1.7: Current Measurement	7
Activity 1.8: Fritzing for 4 switches & LEDS	9
Activity 1.9: Fritzing for Number 0-7	10
Workbook 2	11
Activity 2.1: LED Flashing to show decimal number 63 as binary.	11
Activity 2.2: 4 LED's for counting up in binary from 0 to 15.	12
Activity 2.3: Traffic Lights	15
Workbook 3	17
Activity 3.1: Circuit Diagram of Button & LED	17
Activity 3.2: 3 Switches & Led	19
Activity 3.3: 8 Buttons & LEDs (SWITCH STATEMENTS)	21
Workbook 4	23
Activity 4.1: Serial Port	23
Activity 4.2: Serial Port binary to decimal	26
Activity 4.3: Calibrating Analogue Information	28
Activity 4.4: Temperature Sensor & Serial Port	31
Workbook 5	33
Activity 5.1: RGB Led and switches	33
Activity 5.2: Distance Sensor	35
Activity 5.3: 1602 LCD Display	37
Workbook 6	40
Activity 6.1: PWM	40

Workbook 7	42
Activity 7.1: 2 Arduinos – using Digital Pins	42
Activity 7.2: 2 Arduinos – using Serial I/O	44
Workbook 8	46
Activity 8.1: Stepper Motor Circuit Diagram	46
Activity 8.2: 2 Stepper Motors	48
Workbook 9	49
Activity 9.1: Windscreen Wiper Code using Servos & Temperature Sensor	49
Individual Project (50%)	51
Rationale	51
Timescales	51
Equipment	51
The Project	51
Step 1 produce a detailed description of your project.	51
Step 2 Circuit Diagram & Fritzing Schematic	51
Step 3 A Program	52
Step 4 Testing	52
Step 5 Conclusions	52
Layout	52
Marking	52
All sections carry equal marks.	52

If you prefer, you may use Tinkercad to show a component layout, rather than a circuit Diagram in Fritzing or other circuit design software, though a circuit diagram is more useful as this is what you would most likely see if you were working on embedded systems.

## Workbook 1

### Activity 1.1: Actual voltage across 5V breadboard pins.

5V

### Activity 1.2: Actual voltage across 3.3V breadboard pins.

3.3V

Explain in around 100 words why you think the value read by a multi meter on a circuit, may be different to a simulator value such as TinkerCad.

There is no tolerance to affect the circuit because TinkerCad is not impacted by any external elements like heat, temperature, internal resistance, etc. However, due to internal wire resistance in the multimeter, this is not possible. Additionally, temperature and heat play important roles in developing tolerance. This explains why values in Tinkercad and values obtained from a multimeter are different.

If the read value is 4.84V on a 5V supply, what would be a sensible tolerance to quote, explain your answer.

Actual value in Circuit (a) =4.84V

Labelled value (I) =5v

Tolerance =  $(I-a)/I \times 100$

=3.2%

### Activity 1.3: Potential Divider Calculations

Show the working on how you achieved 2.5V

2.5v can be achieved by using two resistors of same resistance and connect them in the series as resistors when connected in series act as potential divider. As we have used resistors of same resistance, the voltage is divided equally and we can get 2.5v

In calculation;

We have:

Volt=5v


Resistance in one volt=1=220ohm

Total resistance=220+220=440ohm

V after=(R/R total)\*V

=(220/440)\*5

V=2.5v

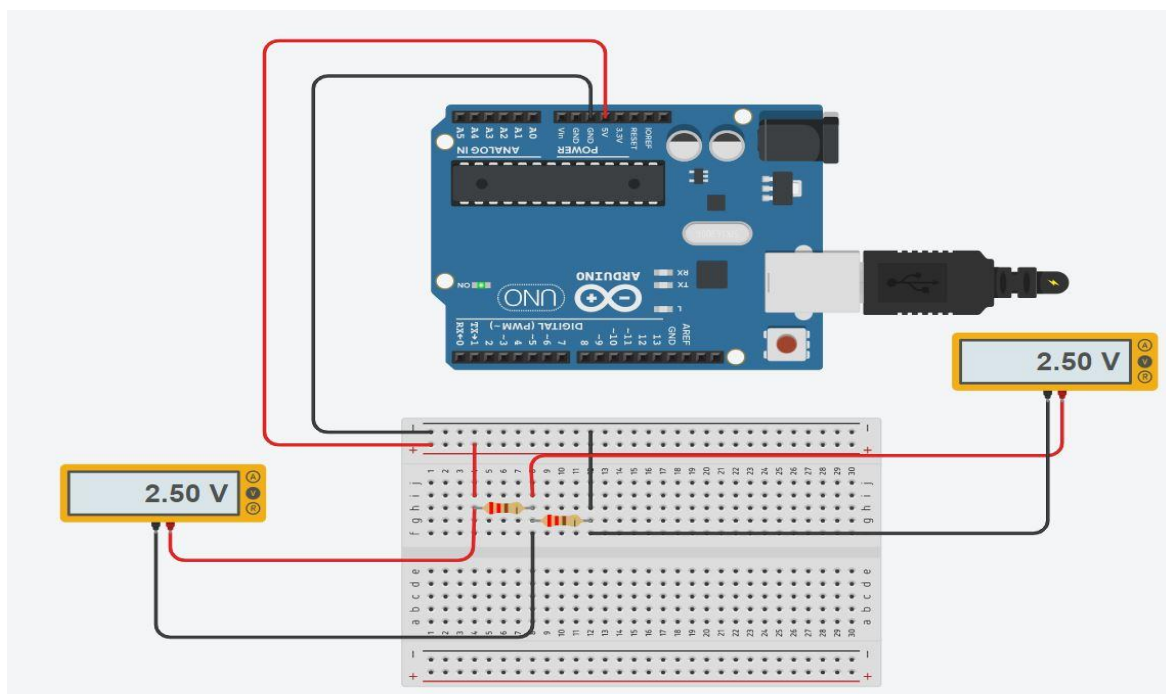

### Activity 1.4: 3V Calculations from either the 5V supply or 3.3V supply

Since the potential drop is 5v and we have 3v drop through one resistor and so simply the other must have 2v drop

Voltage (V1) =3v

Resistance=220ohm

Current (I) =?

We have,

$V1=IR$

$I=V1/r$

So  $I=3/220$


Since, the current flowing through both the resistor would be same;

$V2=IR2$


$2= (3/220) * R2$

$R2=146.67$

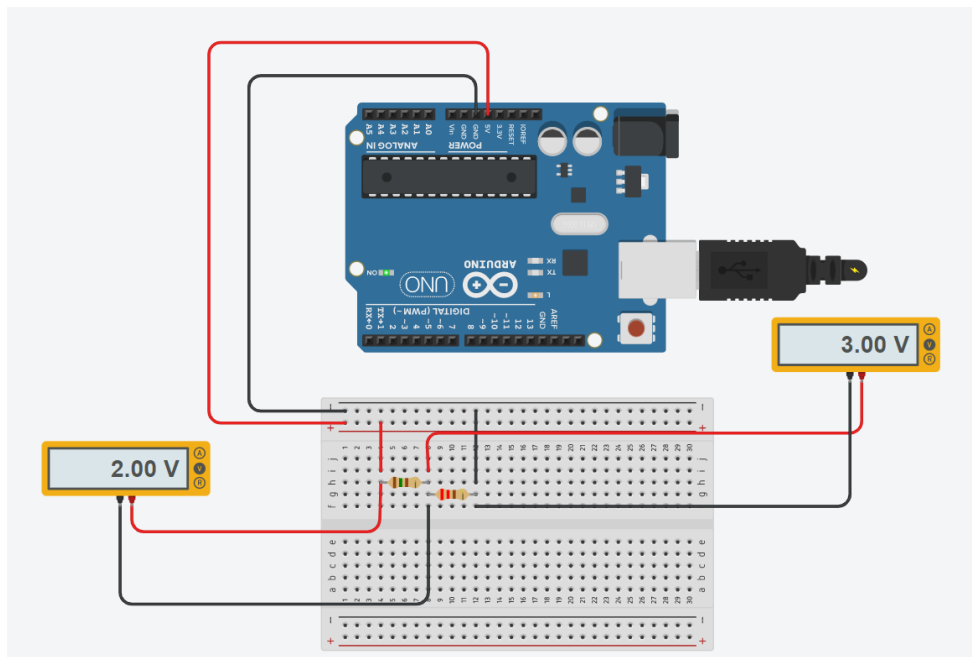So we can use one resistor of resistance 220ohm and another of approximately 146.47ohm to get the 3v and 2v drop through R1 and R2 respectively.


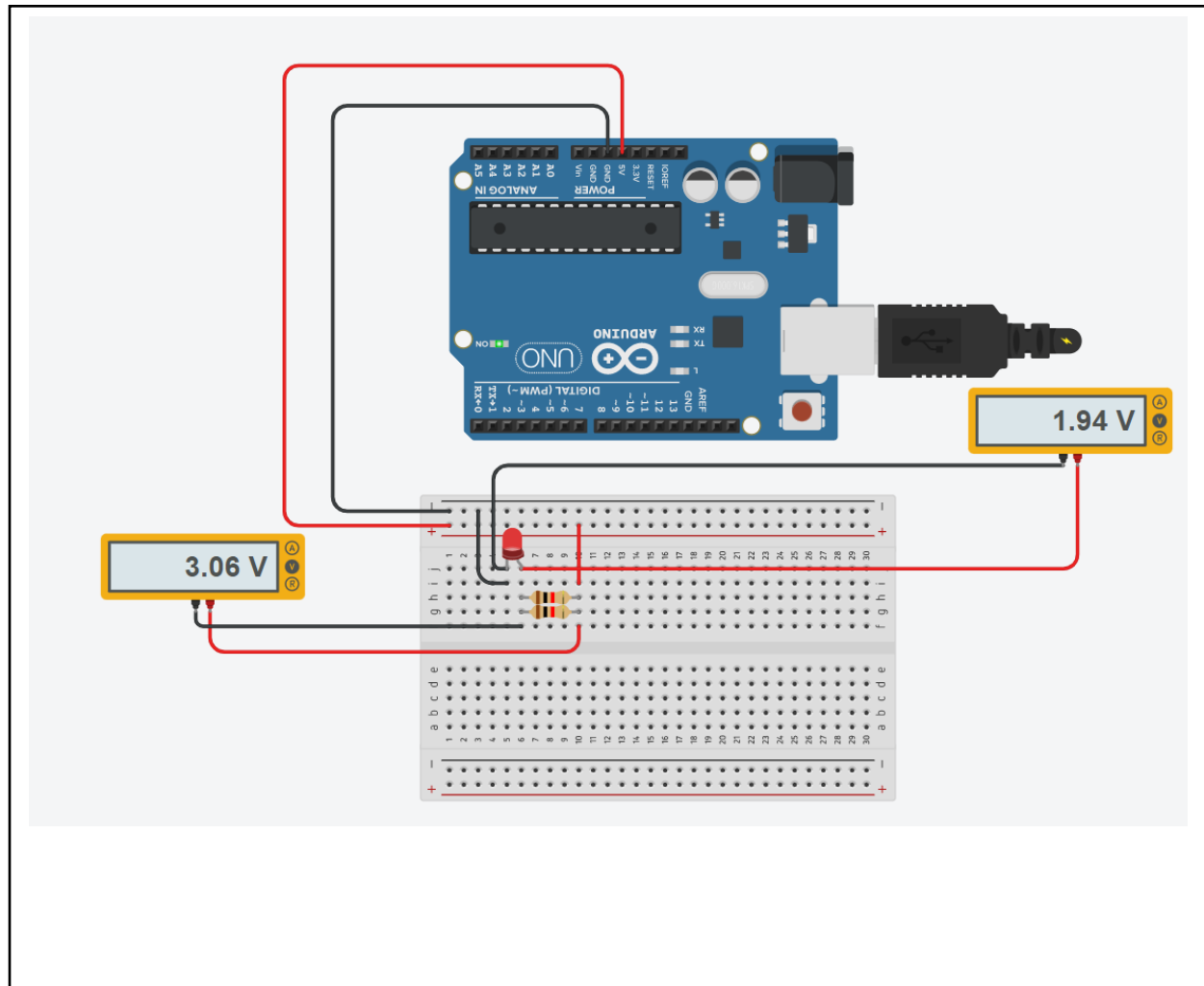
### Activity 1.5: Voltage Divider circuit readings from Breadboard circuit.



## Activity 1.6: LED Circuits

Each resistor Value

220 ohm

220 ohm

Total resistance Calculation

Here,  $R_1=220\text{ ohm}$ , and  $R_2=220\text{ ohm}$ .

Now,

$$1/R = 1/R_1 + 1/R_2$$

$$1/R = 1/220 + 1/220$$

$$1/R = 2/220$$

$$R = 110\text{ohm}$$

Measured Resistance

$R=109\text{ohm}$

If measured resistance is not the same, why not? If you simulated this, why might the real value be different.

Temperature is influenced by the resistance, which makes the resistance tolerant. We can assert that the simulation depicts the actual value even though losses happen in practice and cause the value to deviate from the original value because no external or internal losses are noticed.



## Activity 1.7: Current Measurement

Calculation of current flowing into LED

45 mA

Actual measured value of current

45 mA


Why might they be different?

Known to us


$V=IR$

Therefore, resistivity may change as a result of internal resistance when we measure the current, changing the value of the current as well.
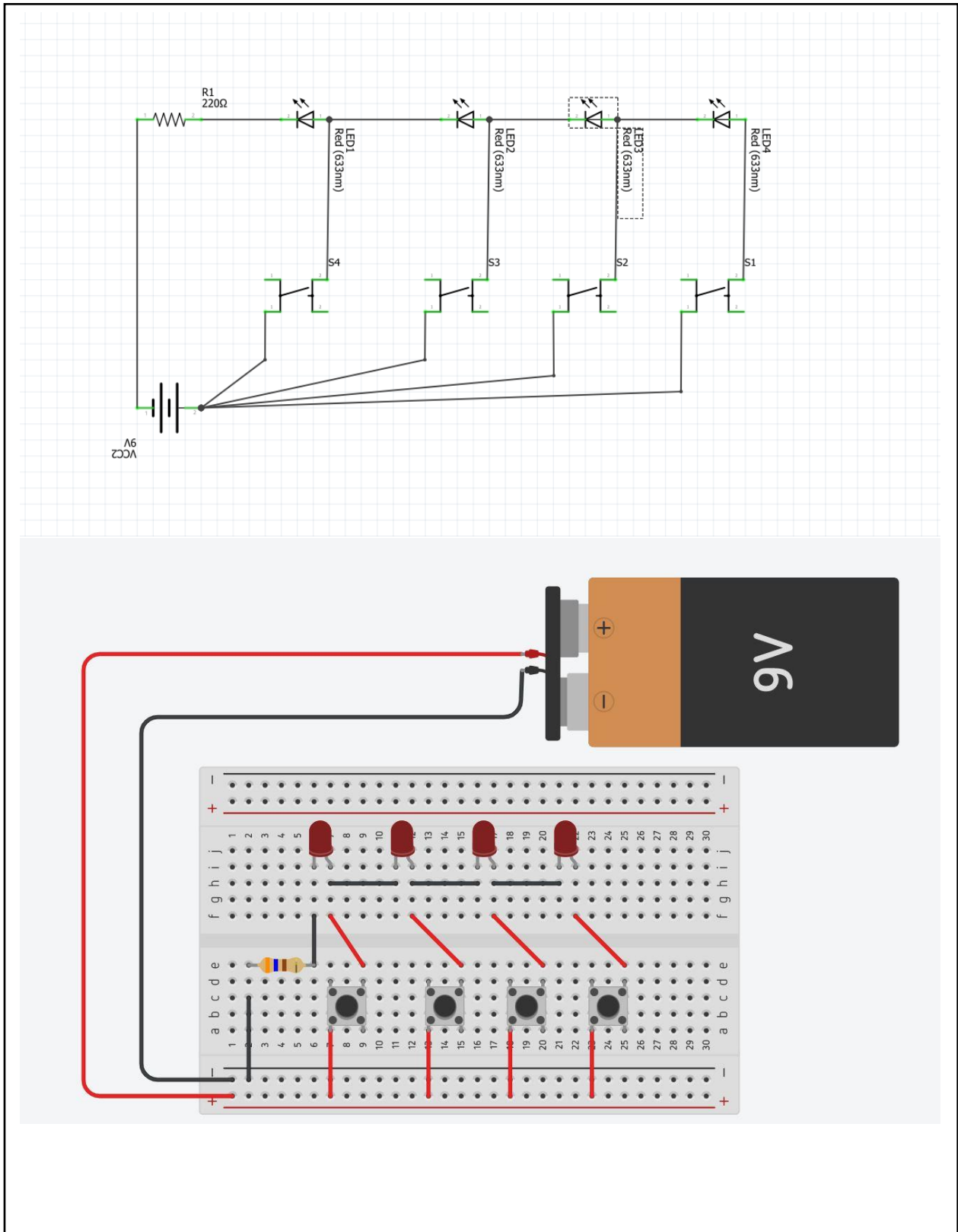
## Activity 1.8: Fritzing for 4 switches & LEDs




## Activity 1.9: Fritzing for Number 0-7

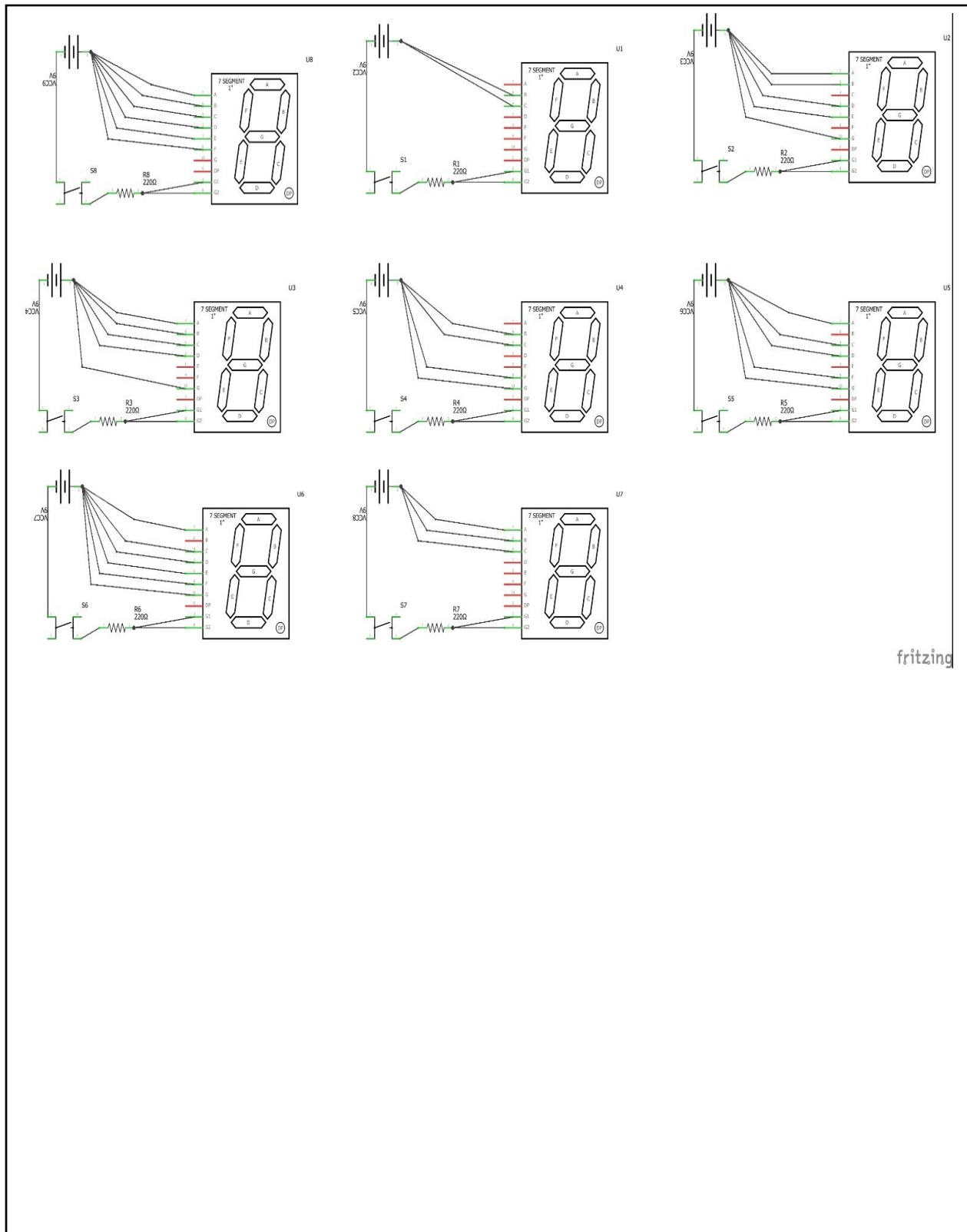

## Workbook 2

### Activity 2.1: LED Flashing to show decimal number 63 as binary.

63 as binary, including working

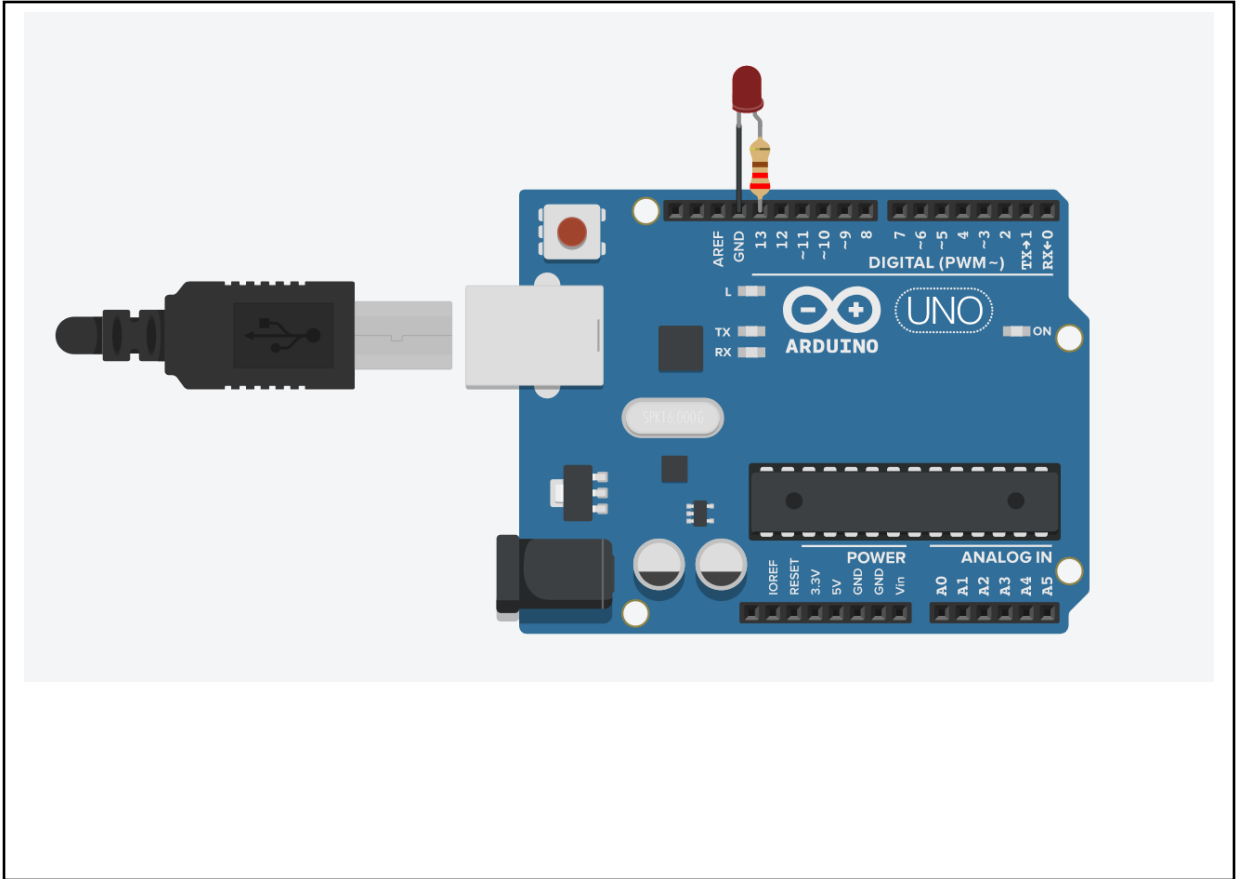

Copy & Post your code with a suitable comment at the top of code with your name & student number

```
/*Binary code for 63 is 111111, meaning the led must be high six times in a row.
```

```
(Divide 63 by 2 and write the remainder from bottom to top)
```

```
Using one LED and one resistor of resistance 220 ohm
```

```
Nayan Raj Khanal
```

```
2227486
```

```
*/
```

```
void setup()
```

```
{
```

```
pinMode(LED_BUILTIN, OUTPUT); // Initializing pin 13 as output pin
```

```
}
```

```
void loop()
```

```
{
```

```
for(int i=0;i<6;i++) //blink LED 6 times
```

```
{
```

```
digitalWrite(LED_BUILTIN, HIGH); //Turning ON LED at Pin 13
```

```
delay(1000); // Wait for 1000 millisecond(s)
```

```
digitalWrite(LED_BUILTIN, LOW); //Turning OFF LED at Pin 13
```

```
delay(1000); // Wait for 1000 millisecond(s)
```

```
}
```


```
delay(5000); // Wait for 5000 millisecond(s)
```

```
}
```


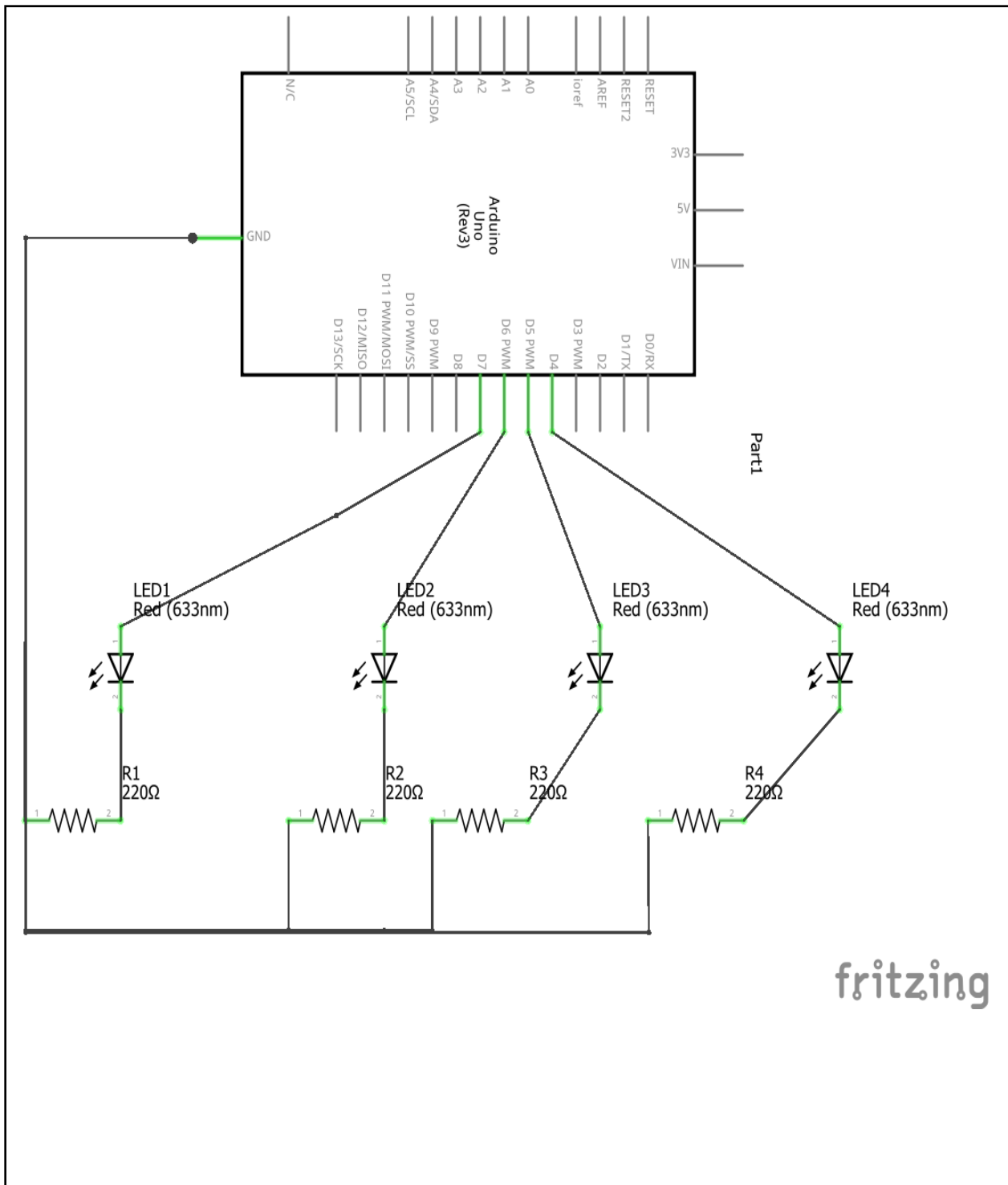
## Activity 2.2: 4 LED's for counting up in binary from 0 to 15.

Fritzing Circuit diagram for Step 4 i.e. 4 LEDs



```
A // C++ code
//Nayan Raj Khanal
//2227486

int ledOne = 13;
int ledTwo = 12;
int ledThree = 11;
int ledFour = 10;

void setup()
{
    pinMode(ledOne, OUTPUT); // Initializing pin 13 as output pin
    pinMode(ledTwo, OUTPUT); // Initializing pin 12 as output pin
    pinMode(ledThree, OUTPUT); // Initializing pin 11 as output pin
    pinMode(ledFour, OUTPUT); // Initializing pin 10 as output pin
}


void ledOn(int a,int b,int c,int d){
    digitalWrite(ledOne, a);
    digitalWrite(ledTwo, b);
    digitalWrite(ledThree, c);
    digitalWrite(ledFour, d);
    delay(1000);
    digitalWrite(ledOne, 0);
    digitalWrite(ledTwo, 0);
    digitalWrite(ledThree, 0);
    digitalWrite(ledFour, 0);
    delay(1000); // Wait for 1000 millisecond(s)
```

```
void loop()
{
  ledOn(0,0,0,0);
  ledOn(0,0,0,1);
  ledOn(0,0,1,0);
  ledOn(0,0,1,1);
  ledOn(0,1,0,0);
  ledOn(0,1,0,1);
  ledOn(0,1,1,0);
  ledOn(0,1,1,1);
  ledOn(1,0,0,0);
  ledOn(1,0,0,1);
  ledOn(1,0,1,0);
  ledOn(1,0,1,1);
  ledOn(1,1,0,0);
  ledOn(1,1,0,1);
  ledOn(1,1,1,0);
  ledOn(1,1,1,1);
}
```


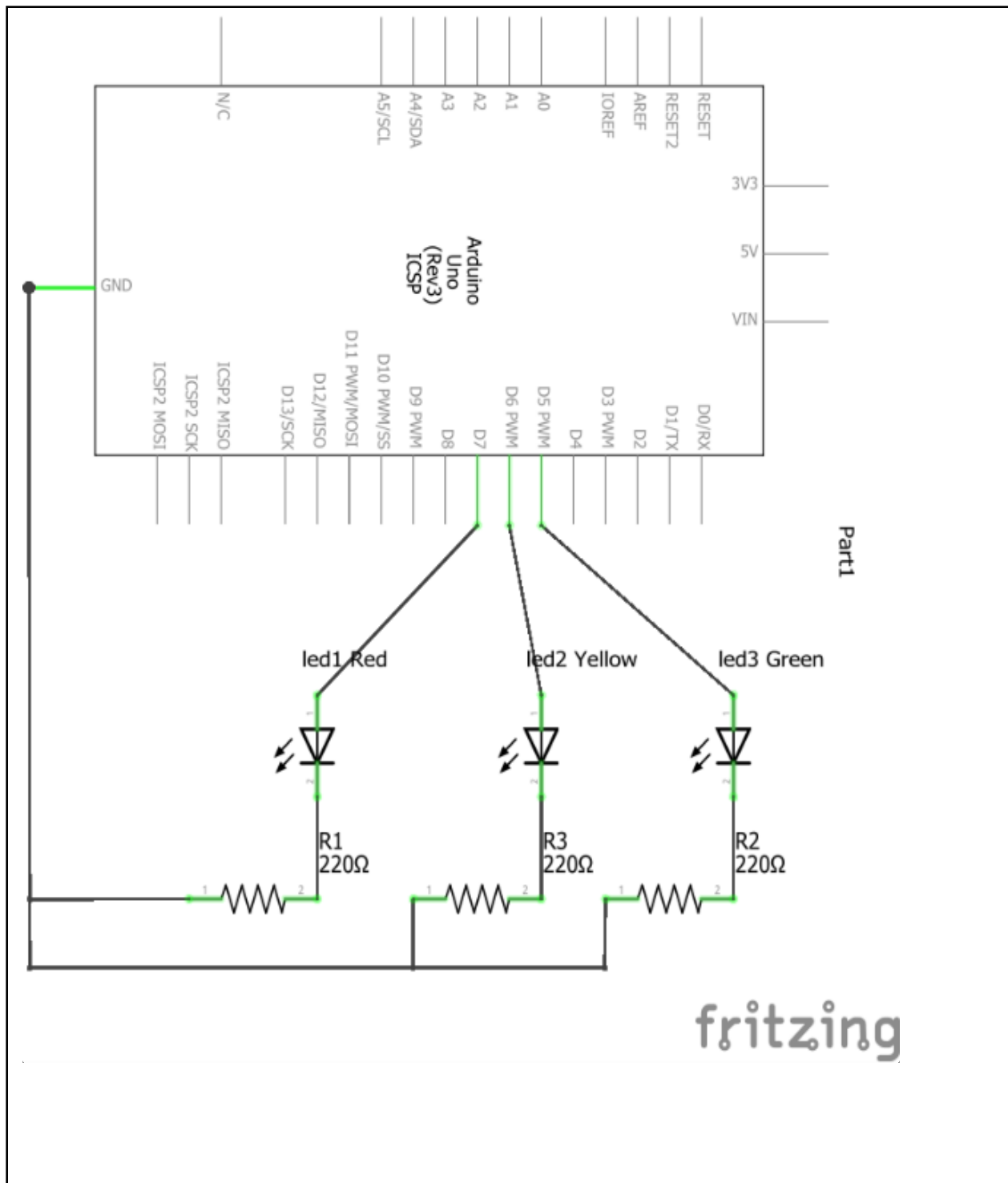
## Activity 2.3: Traffic Lights

Fritzing Circuit diagram for Step 4 i.e. 4 LEDs



#### Arduino Program for Step 4 i.e. 4 LEDs

//Name:Nayan Raj Khanal

//ID: 2227486

int GREEN = 8;

int YELLOW = 9;

int RED = 10;

int DELAY\_GREEN = 5000;

int DELAY\_YELLOW = 2000;

int DELAY\_RED = 5000;

// basic functions

void setup()

{

pinMode(GREEN, OUTPUT); **// Initializing GREEN as output pin**

pinMode(YELLOW, OUTPUT); **// Initializing YELLOW as output pin**

pinMode(RED, OUTPUT); **// Initializing RED as output pin**

}

void loop()

{

green\_light();

delay(DELAY\_GREEN);

yellow\_light\_2();

delay(DELAY\_YELLOW);

red\_light();

delay(DELAY\_RED);

yellow\_light();

delay(DELAY\_YELLOW);

```
void red_light()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, LOW);
    digitalWrite(RED, HIGH);
}

void green_light()
{
    digitalWrite(GREEN, HIGH);
    digitalWrite(YELLOW, LOW);
    digitalWrite(RED, LOW);
}

yellow_light();
    delay(DELAY_YELLOW);

}
```

```
void red_light()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, LOW);
    digitalWrite(RED, HIGH);
}

void green_light()
{
    digitalWrite(GREEN, HIGH);
    digitalWrite(YELLOW, LOW);
    digitalWrite(RED, LOW);
}
```

```
void yellow_light()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, HIGH);
    digitalWrite(RED, HIGH);
}
```

```
void yellow_light_2()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, HIGH);
    digitalWrite(RED, LOW);
}
```


```
void yellow_light()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, HIGH);
    digitalWrite(RED, HIGH);
}
```

```
void yellow_light_2()
{
    digitalWrite(GREEN, LOW);
    digitalWrite(YELLOW, HIGH);
    digitalWrite(RED, LOW);
}
```

## Workbook 3

### Activity 3.1: Circuit Diagram of Button & LED

Fritzing

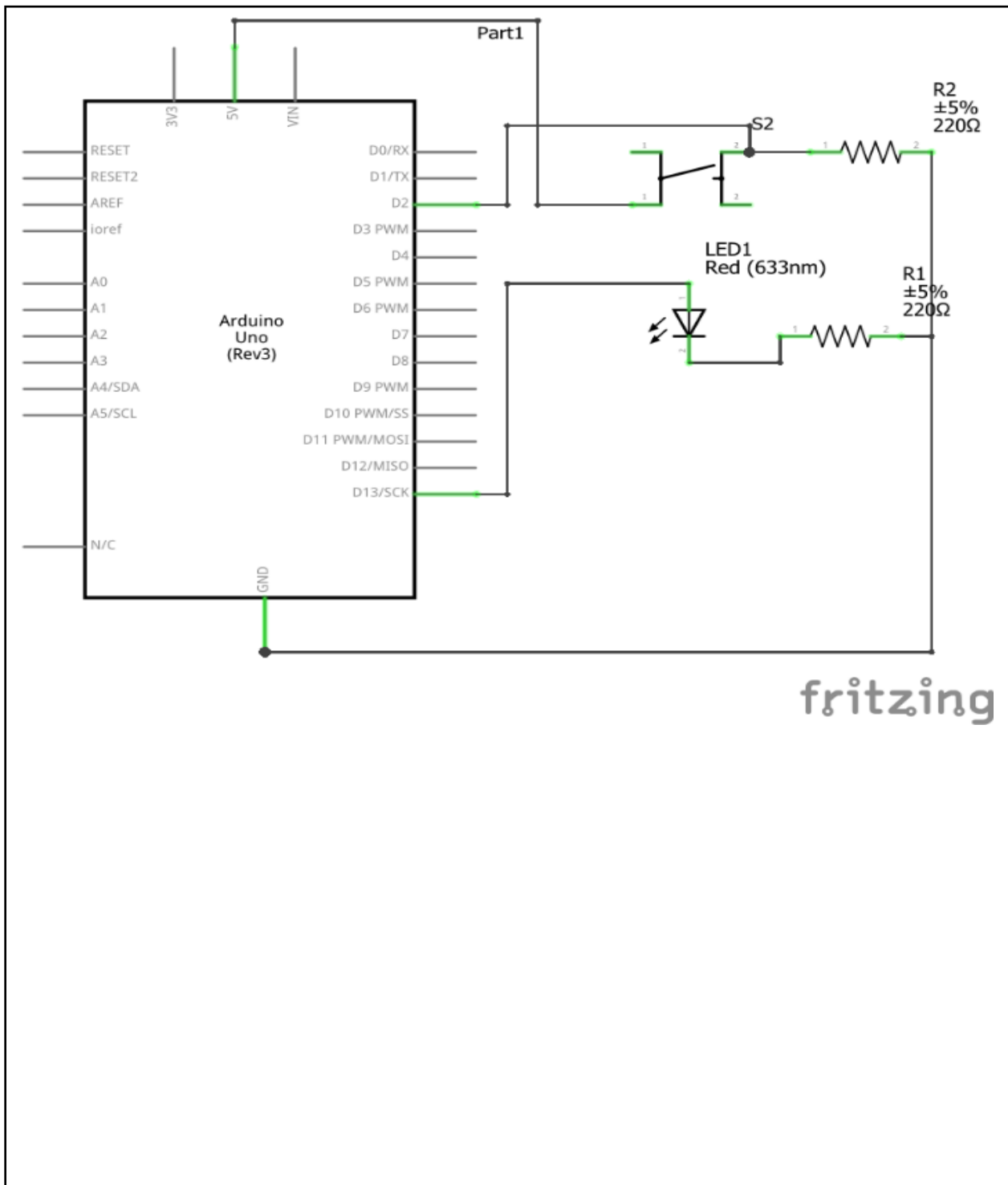


## Arduino Program

```
/*  
C++ code  
Nayan Raj Khanal  
2227486  
This program employs a pull-up resistor with an extra-large capacity to cut down on self-generated  
electrical noise.  
*/  
  
int buttonPin =2;  
int Ledpin=13;  
void setup()  
{  
  pinMode(2, INPUT); // Initializing pin 2 as input pin  
  pinMode(13, OUTPUT); // Initializing pin 13 as output pin  
}  
  
void loop()  
{  
  int input=digitalRead(2);  
  if (input ==HIGH){  
    digitalWrite(13,HIGH);  
  
  }  
  else {  
    digitalWrite(13,LOW);  
  }  
}
```

## Activity 3.2: 3 Switches & Led

### Fritzing Circuit Diagram

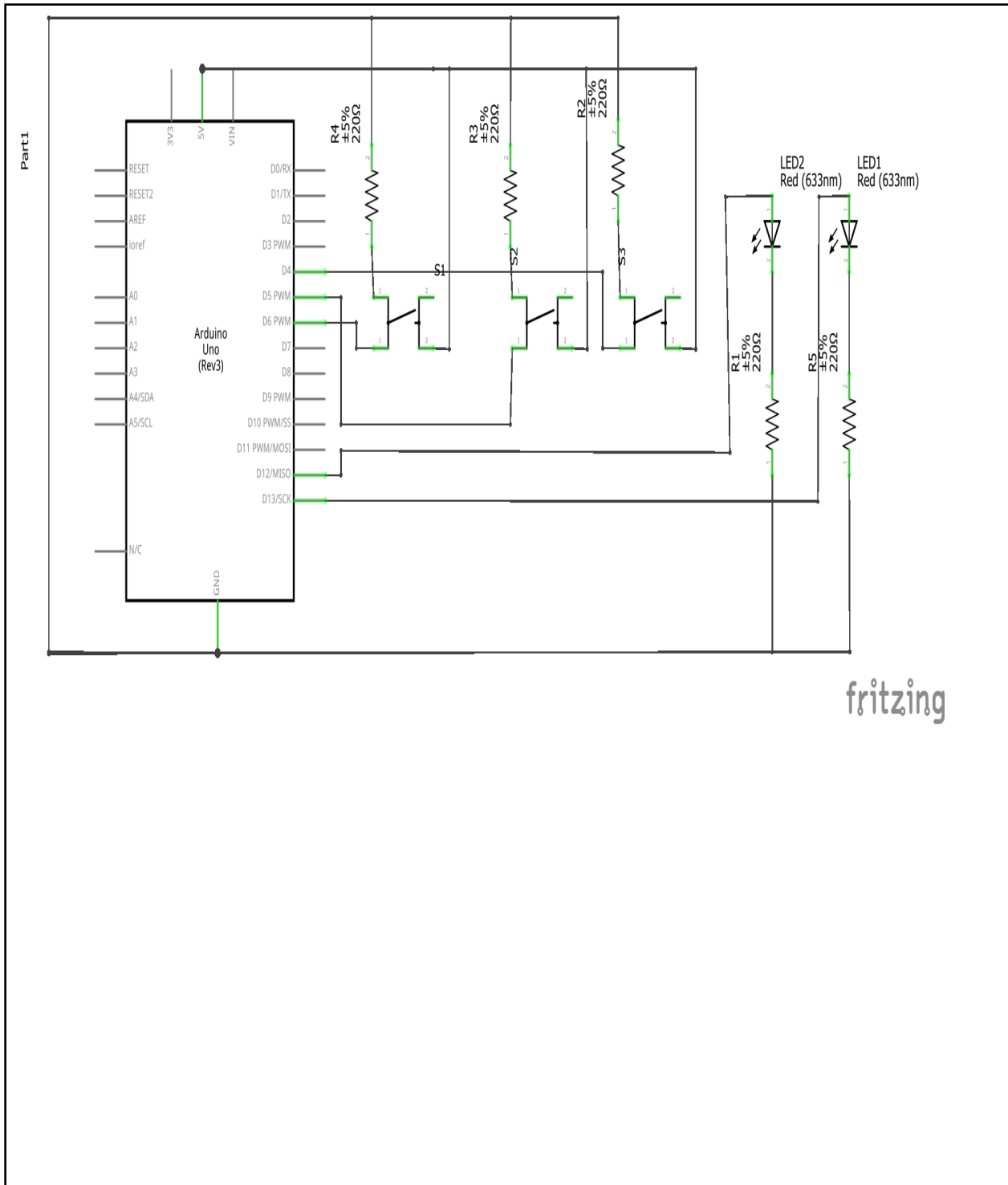

```
//Name:Nayan Raj Khanal
```

```
//ID: 2227486
```

```
int redLed = 13;
```

```
int blueLed = 12;
```

```
int switch1 = 6;
```

```
int switch2 = 5;
```

```
int switch3 = 4;
```

```
void setup()
```

```
{
```

```
  pinMode(redLed, OUTPUT); // Initializing redLed as output pin
```

```
  pinMode(blueLed, OUTPUT); // Initializing blueLed as output pin
```

```
  pinMode(switch1, INPUT); // Initializing switch1 as input pin
```

```
  pinMode(switch2, INPUT); // Initializing switch2 as input pin
```

```
  pinMode(switch3, INPUT); // Initializing switch3 as input pin
```

```
}
```

```
void loop()
```

```
{
```

```
  int switchState1 = digitalRead(switch1);
```

```
  int switchState2 = digitalRead(switch2);
```

```
  int switchState3 = digitalRead(switch3);
```

```
  if(switchState1 == HIGH){
```

```
    digitalWrite(13, HIGH);
```

```
    delay(1000);
```

```
    digitalWrite(13, LOW);
```


```
}
```



```
else if(switchState2 == HIGH){  
    digitalWrite(12, HIGH);  
    delay(2000);  
    digitalWrite(12, LOW);  
}  
  
else if(switchState3 == HIGH){  
    digitalWrite(13, HIGH);  
    delay(3000);  
    digitalWrite(13, LOW);  
}  
}
```

### Activity 3.3: 8 Buttons & LEDs (SWITCH STATEMENTS)

Fritzing

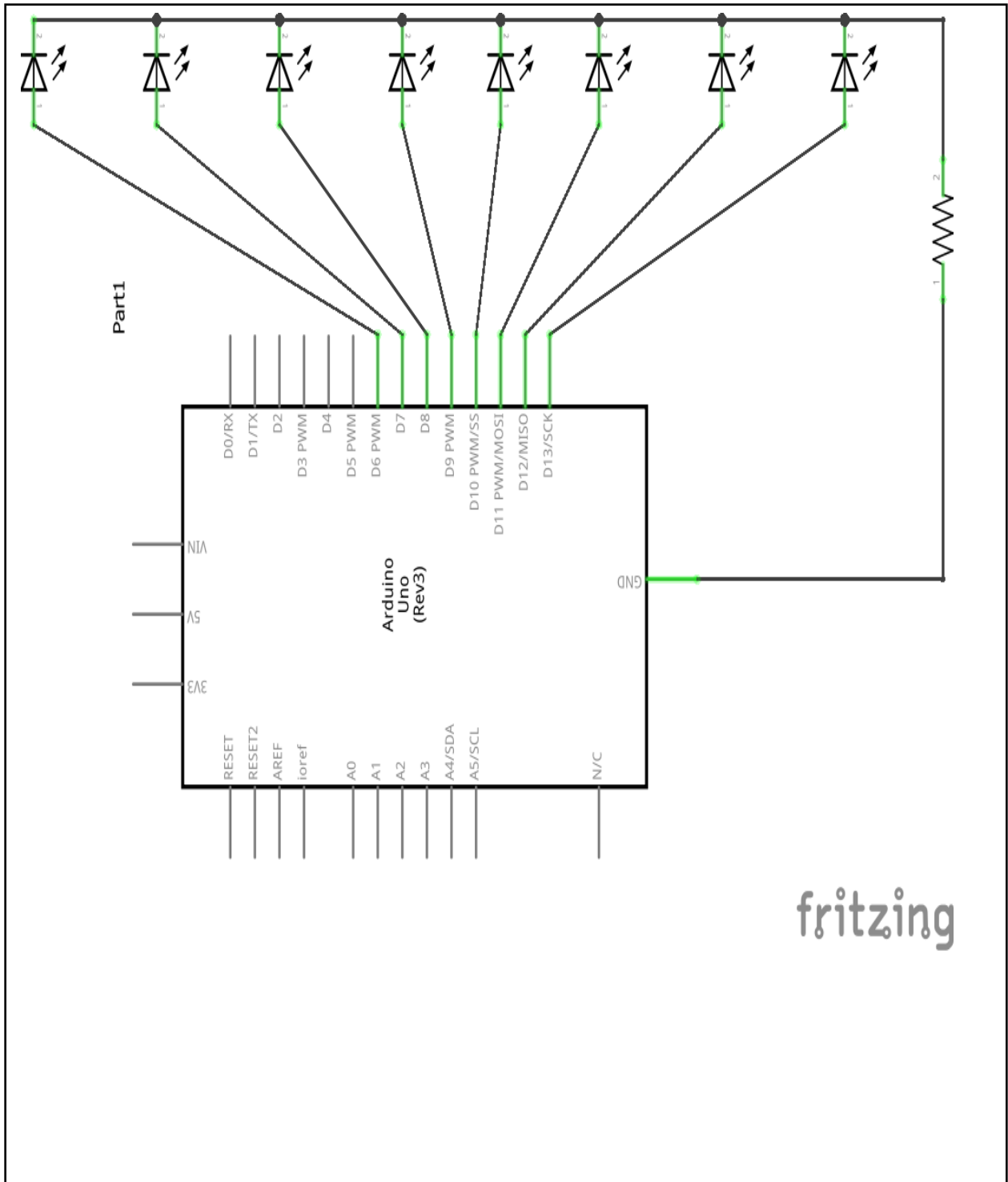

## Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486

int binaryNumber[8];

void setup()
{
    pinMode(13, OUTPUT); // Initializing pin 13 as output pin
    pinMode(12, OUTPUT); // Initializing pin 12 as output pin
    pinMode(11, OUTPUT); // Initializing pin 11 as output pin
    pinMode(10, OUTPUT); // Initializing pin 10 as output pin
    pinMode(9, OUTPUT); // Initializing pin 9 as output pin
    pinMode(8, OUTPUT); // Initializing pin 8 as output pin
    pinMode(7, OUTPUT); // Initializing pin 7 as output pin
    pinMode(6, OUTPUT); // Initializing pin 6 as output pin
    Serial.begin(9600);
}

void displayOutput(int value) {
    for(int i = 0; i<9; i++){
        binaryNumber[i] = value % 2;
        value = value/2;
    }
    digitalWrite(13, binaryNumber[7]);
    digitalWrite(12, binaryNumber[6]);
    digitalWrite(11, binaryNumber[5]);
    digitalWrite(10, binaryNumber[4]);
    digitalWrite(9, binaryNumber[3]);
    digitalWrite(8, binaryNumber[2]);
```

```
digitalWrite(7, binaryNumber[1]);
```

```
    digitalWrite(6, binaryNumber[0]);
```

```
}
```

```
void loop()
```

```
{
```

```
    displayOutput(111);
```


```
    exit(0);
```

```
}
```


## Workbook 4

### Activity 4.1: Serial Port

Fritzing

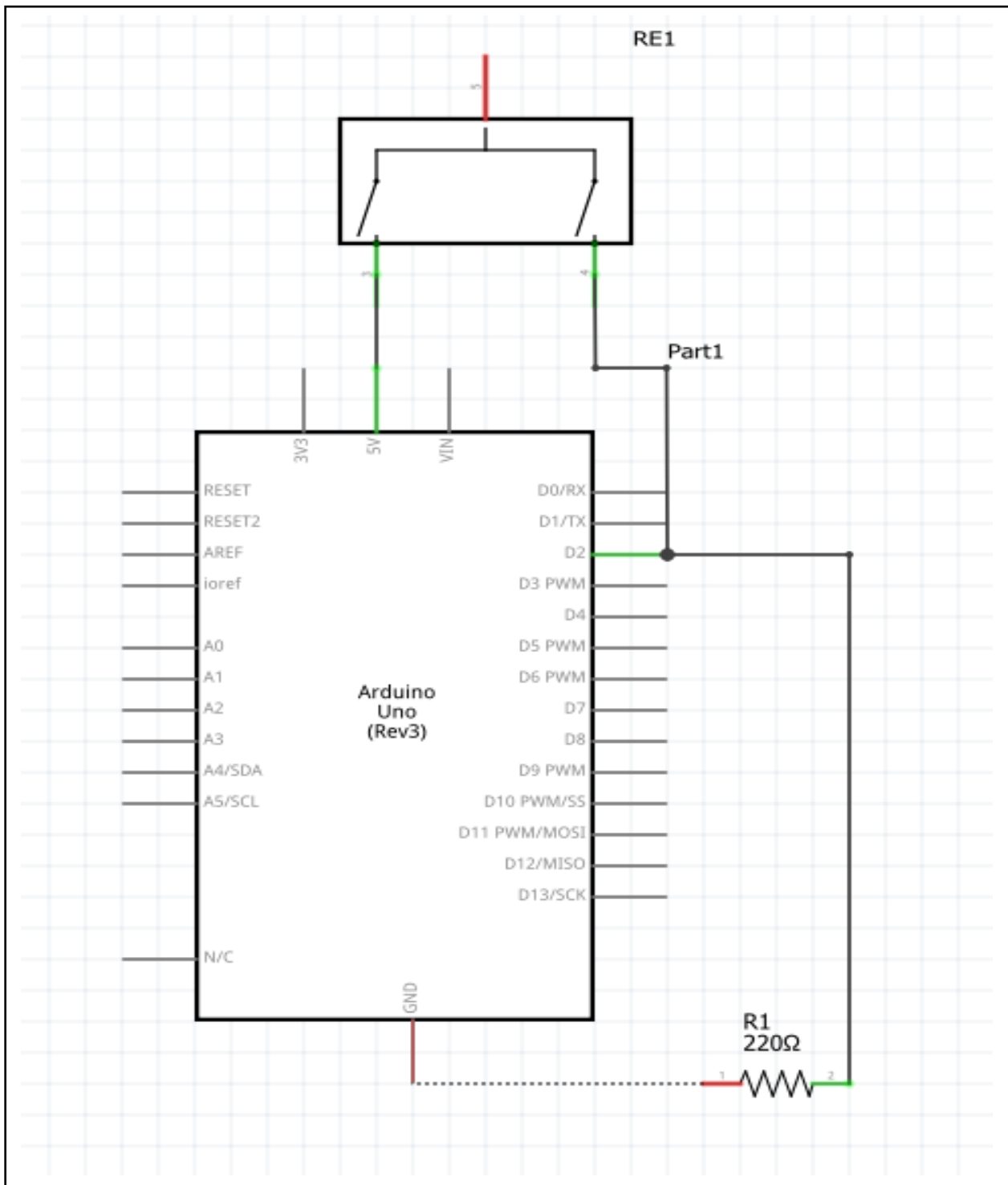


## Arduino Program

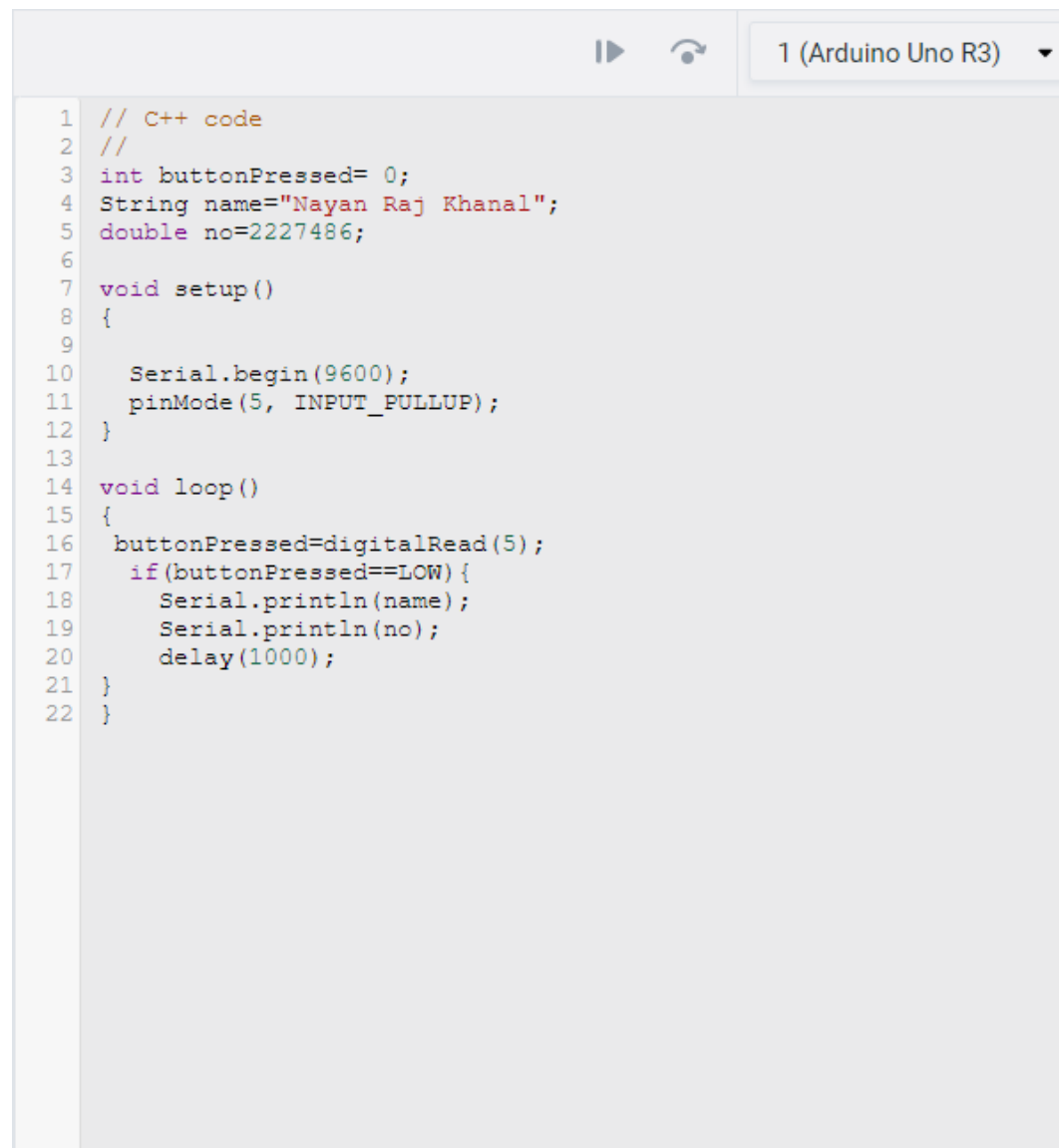The image shows a screenshot of the Arduino IDE interface. At the top, there is a toolbar with a play button (upload) and a circular arrow button (refresh/reset). To the right of the toolbar, a dropdown menu shows '1 (Arduino Uno R3)'. The main area of the IDE contains a C++ code file with 22 lines. The code defines a variable 'buttonPressed' as an integer, a 'name' as a string, and a 'no' as a double. It then defines a 'setup' function to initialize serial communication and pin mode, and a 'loop' function that checks for a button press and prints the name and number to the serial monitor with a delay.


```
1 // C++ code
2 //
3 int buttonPressed= 0;
4 String name="Nayan Raj Khanal";
5 double no=2227486;
6
7 void setup()
8 {
9
10     Serial.begin(9600);
11     pinMode(5, INPUT_PULLUP);
12 }
13
14 void loop()
15 {
16     buttonPressed=digitalRead(5);
17     if(buttonPressed==LOW) {
18         Serial.println(name);
19         Serial.println(no);
20         delay(1000);
21     }
22 }
```

Screen Shot of Serial Port

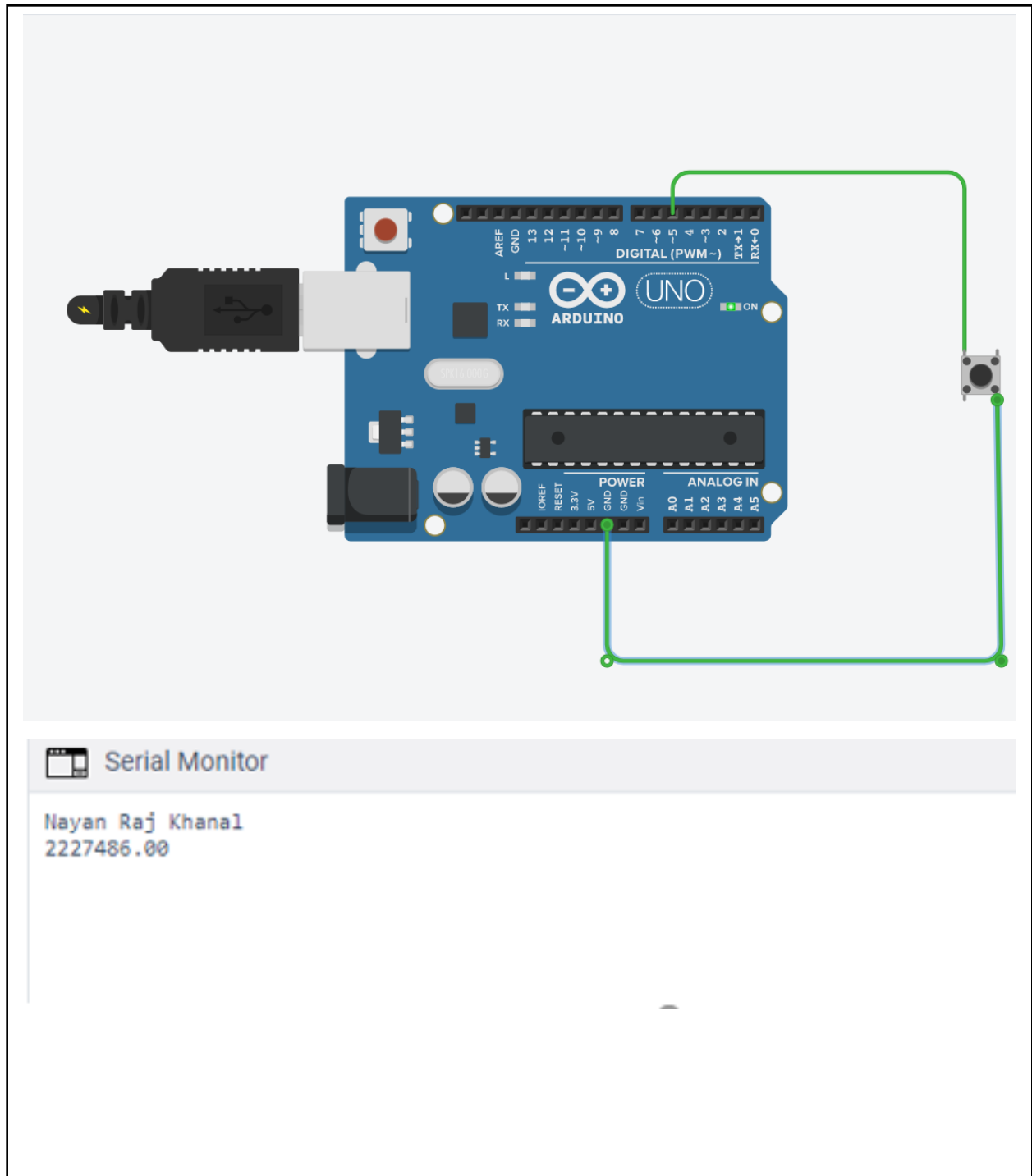

## Activity 4.2: Serial Port binary to decimal

### Code

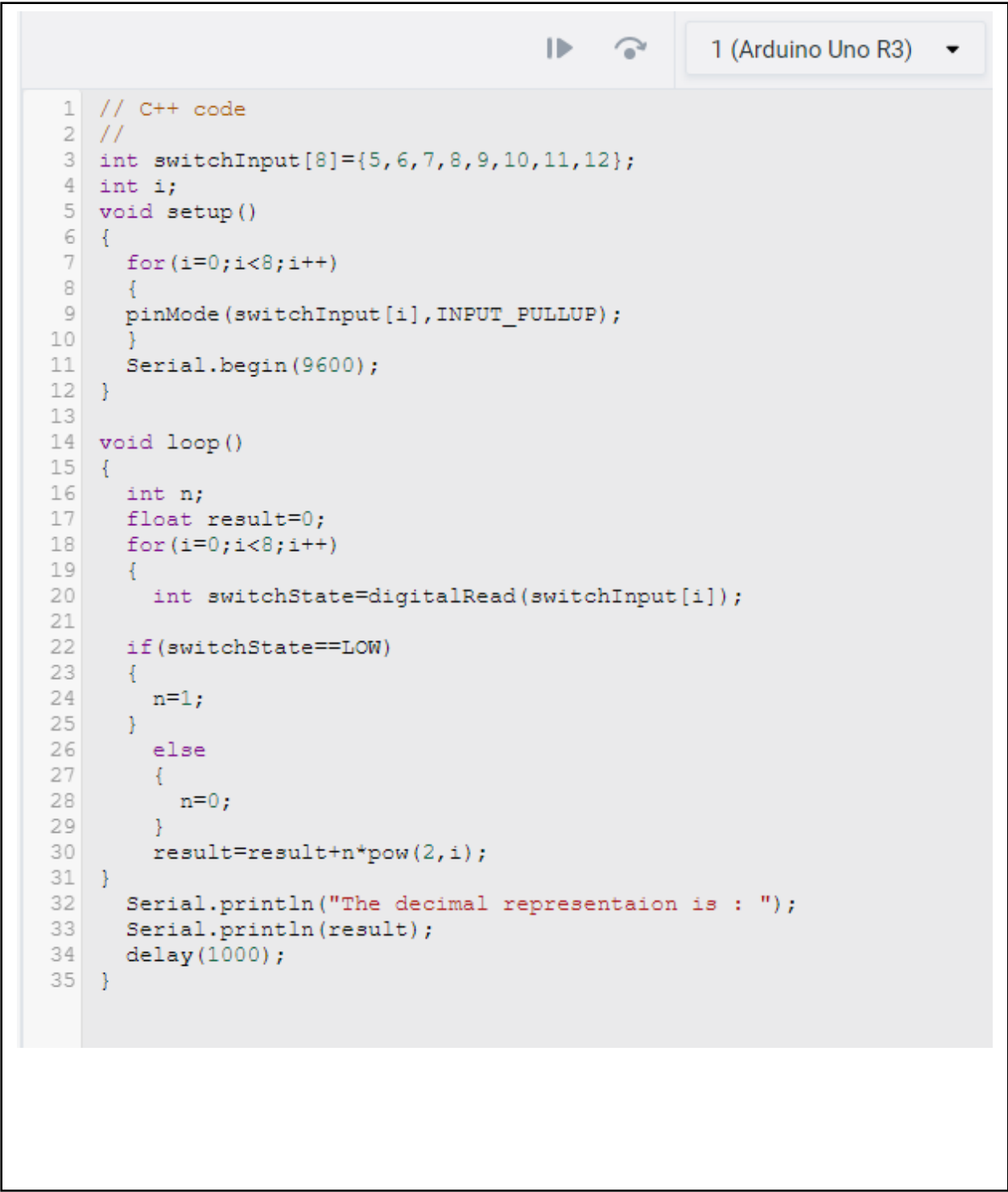


The image shows a screenshot of an Arduino IDE code editor. At the top right, there is a dropdown menu showing "1 (Arduino Uno R3)". The code is written in C++ and is as follows:

```
1 // C++ code
2 //
3 int switchInput[8]={5,6,7,8,9,10,11,12};
4 int i;
5 void setup()
6 {
7     for(i=0;i<8;i++)
8     {
9         pinMode(switchInput[i],INPUT_PULLUP);
10    }
11    Serial.begin(9600);
12 }
13
14 void loop()
15 {
16     int n;
17     float result=0;
18     for(i=0;i<8;i++)
19     {
20         int switchState=digitalRead(switchInput[i]);
21
22         if(switchState==LOW)
23         {
24             n=1;
25         }
26         else
27         {
28             n=0;
29         }
30         result=result+n*pow(2,i);
31     }
32     Serial.println("The decimal representaion is : ");
33     Serial.println(result);
34     delay(1000);
35 }
```



## Screen Shot of Serial Port

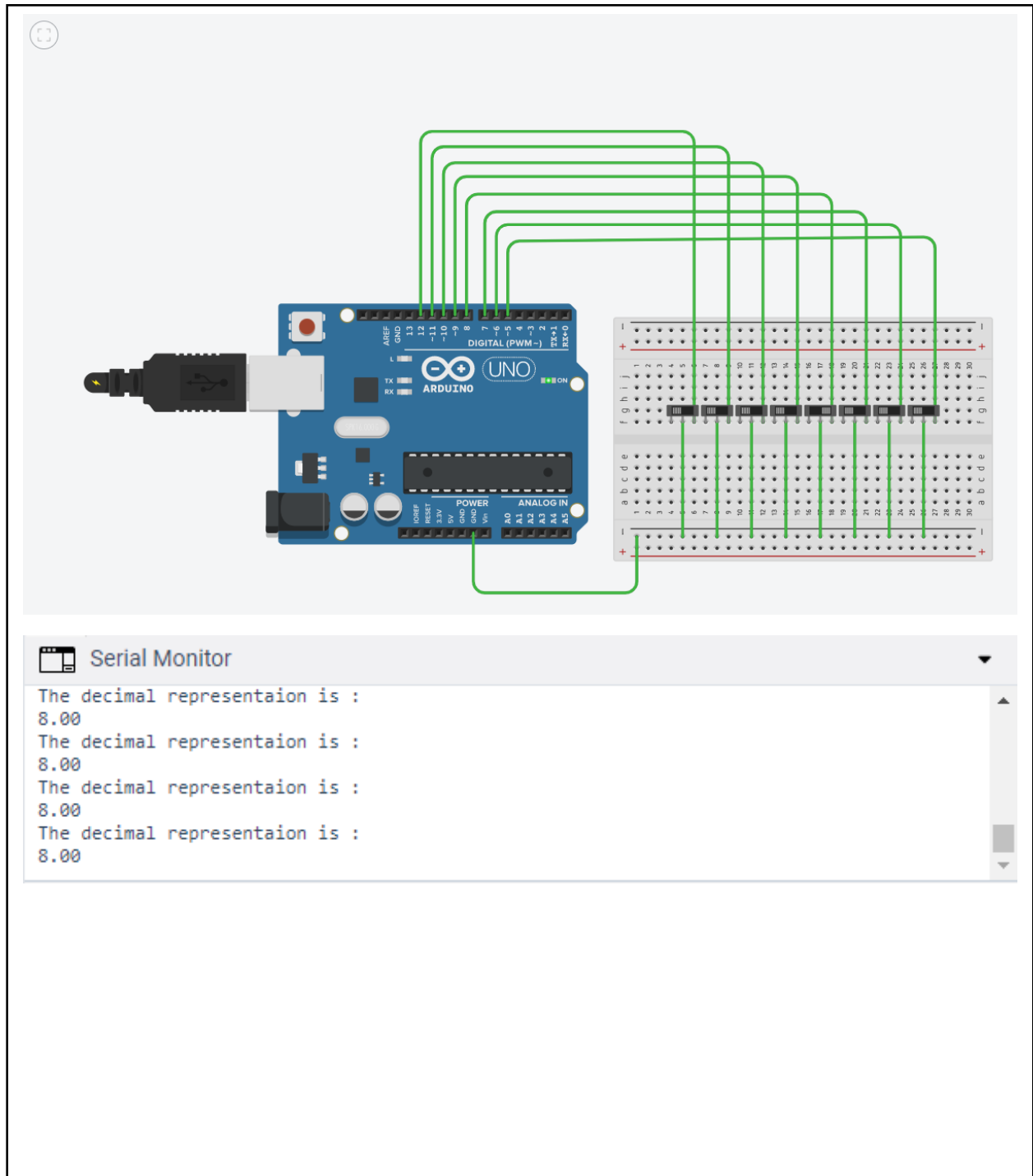

### Activity 4.3: Calibrating Analogue Information

Code

```
//Name:Nayan Raj Khanal
//ID: 2227486

const int buttonPin=2;
int buttonState=0;

void setup()
{
  pinMode(buttonPin, INPUT); // Initializing buttonPin as input
  Serial.begin(9600);
  pinMode(A0,INPUT); // Initializing A0 as input pin
}

void loop()
{
  buttonState=digitalRead(buttonPin);
  if (buttonState==HIGH){
    int sensorValue=analogRead(A0);
    float voltage=sensorValue*(5.0/1024.0);
    Serial.print(voltage);
    Serial.println('V');
    float resistance=(voltage*250)/5;
    Serial.print(resistance);
    Serial.println("KOhm");
    delay(1000);
  }
}
```

Pot Resistance Clockwise

250 KOhm

Pot Resistance Anti-clockwise


0

Sample of Values

Pot Resistance against Voltage change

Pot Resistance	Voltage Measured
209.72KOhm	4.19V
169.92KOhm	3.40V
124.76KOhm	2.50V
84.96KOhm	1.70V
40.04KOhm	0.80V

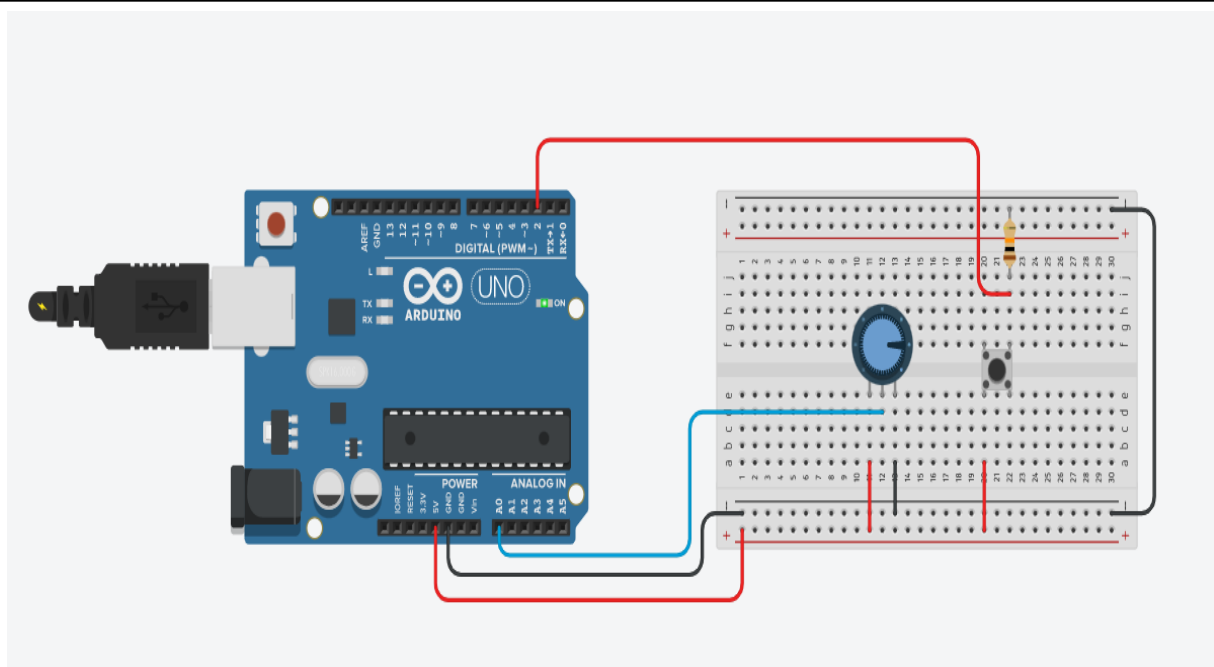Screen Shot of Meaningful Serial Port Output, not just numbers



### Serial Monitor

4.19V  
209.72KOhm  
3.40V  
169.92KOhm  
2.50V  
124.76KOhm  
1.70V  
84.96KOhm  
0.80V  
40.04KOhm

#### Activity 4.4: Temperature Sensor & Serial Port


Code - Centigrade to Serial port, but when button Pressed Fahrenheit Displayed Instead

```
//Name:Nayan Raj Khanal
//ID: 2227486

void setup()
{
  pinMode(A0, INPUT); // Initializing A0 as input pin
  pinMode(2,INPUT); // Initializing pin 2 as input pin
  Serial.begin(9600);
}

void loop()
{
  int btn=digitalRead(2);
  if (btn==HIGH){
    float analogReading = analogRead(A0);
    float degreeCentigrade = (analogReading*500)/1024;
    Serial.print("degreeCentigrade:");
    Serial.println(degreeCentigrade);
    float fahrenheit=degreeCentigrade*1.8+32;
    Serial.print("degreeFahrenheit:");
    Serial.println(fahrenheit);
    delay(3000);
  }
}
```

## Screen Shot of Serial Port

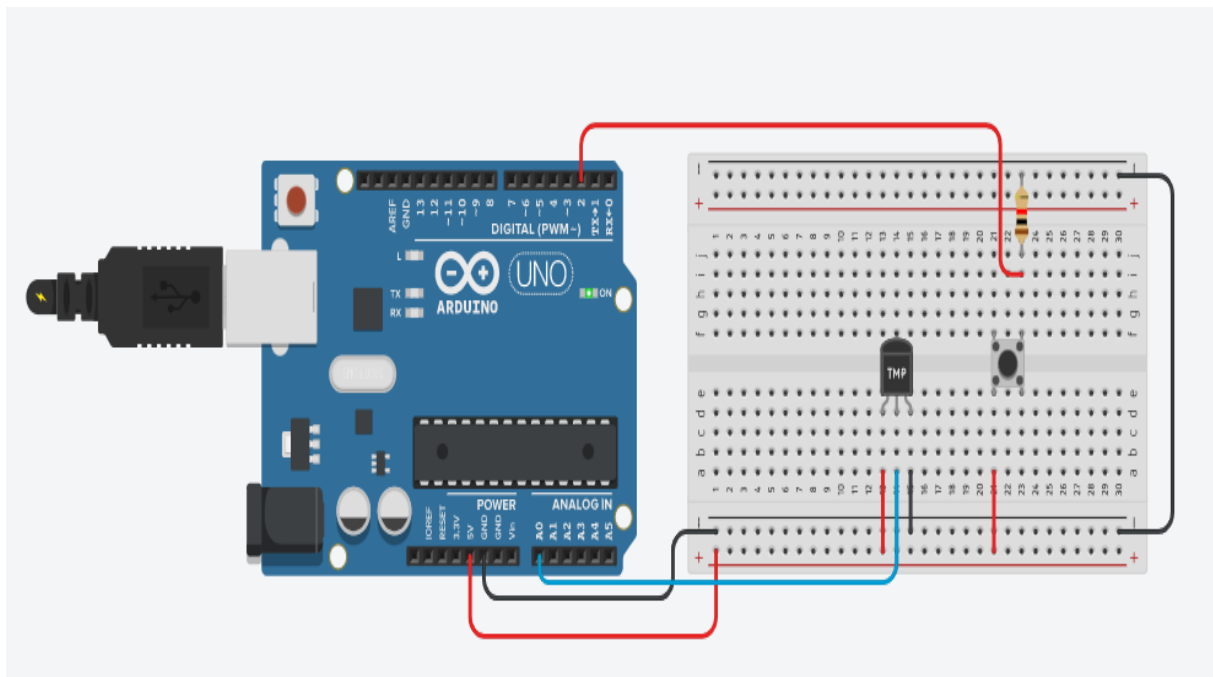


Serial Monitor

```
degreeCentigrade:74.71  
degreeFahrenheit:166.47
```

## Workbook 5

### Activity 5.1: RGB Led and switches

Fritzing

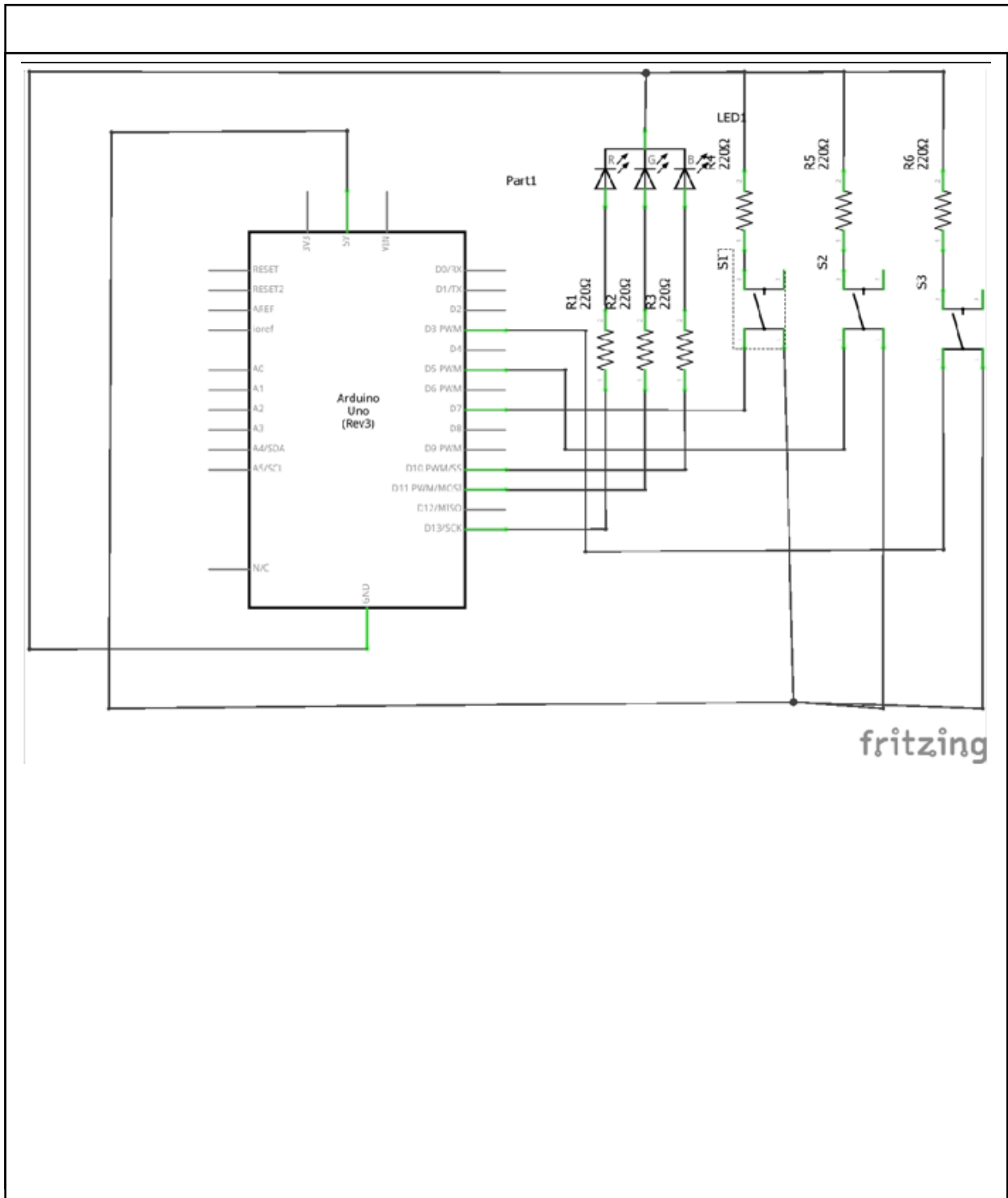

Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486

// C++ code
//

// input value of three led
int red_rgb= 13;// input for red led at pin 13
int blue_rgb= 11; ;// input for blue led at pin 11
int green_rgb= 10; ;// input for green led at pin 10

//three switch are conencted.int switchInput1=7;
int
switchInput2=5
;int
switchInput3=3
;

void setup();// starting the code
{
// setting pin connection to all the led

// voltage set for red blue and green led

pinMode(red_rgb,
OUTPUT);
pinMode(blue_rgb,
OUTPUT);
pinMode(green_rgb,
OUTPUT);

// voltage set for all the
three switch

pinMode(switchInput1,
INPUT);
pinMode(switchInput2,
INPUT);
pinMode(switchInput3,
INPUT);
}

void loop();// starting the loop
```



```
void loop()// starting the loop
{
int switchState1 = digitalRead(switchInput1);// input value is equal to voltage given
int switchState2 = digitalRead(switchInput2) );// input value is equal to voltage given
if (switchState1==HIGH)

{

digitalWrite(red_rgb, HIGH); // voltage setup for red led at High
delay(1000); );// wait for 1000 millisecond
digitalWrite(red_rgb, LOW); // voltage setup for redled at low
delay(1000); );// wait for 1000 millisecond }
if(switchState2==HIGH)
{
digitalWrite(blue_rgb, HIGH); // voltage setup for blue led at High
delay(1000);
digitalWrite(blue_rgb, LOW); // voltage setup for blue led at low
delay(1000); );// wait for 1000 millisecond }
if(switchState3==HIGH)
{
digitalWrite(green_rgb, HIGH); // voltage setup for green led at High
delay(1000); );// wait for 1000 millisecond
digitalWrite(green_rgb, LOW); // voltage setup for green led at low
delay(1000);// wait for 1000 millisecond
}
}
```

## Activity 5.2: Distance Sensor

```
//Name:Nayan Raj Khanal
//ID: 2227486

#define trigPin 7
#define echoPin 3


int redLed=13;
int blueLed=12;
int greenLed=11;

void setup() {
  Serial.begin (9600); //view value received
  pinMode(echoPin, INPUT_PULLUP); // setting pin connection for echo pin
  pinMode(redLed, OUTPUT) ); // setting pin connection for red led
  pinMode(blueLed, OUTPUT); ); // setting pin connection for blue led
  pinMode(greenLed, OUTPUT); ); // setting pin connection for green led
}

void loop() { // starting the loop
  long duration, inches, cm;
  pinMode(trigPin, OUTPUT); // calculate distance from ultrasonic pulse
  digitalWrite(trigPin, LOW);
  delayMicroseconds(2); // wait 2 microsecond
  digitalWrite(trigPin, HIGH); // voltage set for tripin
  delayMicroseconds(10); // wait for 10 macrosecond
  digitalWrite(trigPin, LOW);
  duration = pulseIn(echoPin, HIGH);
  Serial.println(duration); // serial print
  inches = duration/74/2;
  cm = duration/29/2;
```


```
if(cm<200){
  if(cm<40)
  {
    digitalWrite(redLed, HIGH); // voltage set for red led
    delay(1000); // wait 1000 millisecond
    digitalWrite(redLed, LOW);
  }
  if(cm>40 && cm<100)
  {
    digitalWrite(blueLed, HIGH); // voltage set for blue led
    delay(1000); // wait 1000 millisecond
    digitalWrite(blueLed, LOW);
  }
  if(cm>100)
  {
    digitalWrite(greenLed, HIGH); // voltage set for greenled
    delay(1000); // wait 1000 millisecond
    digitalWrite(greenLed, LOW);
  }
}
Serial.println(cm); //view value used from ultrasonic pulse
delay(1000); // wait for a second 1000 millisecond
}
```

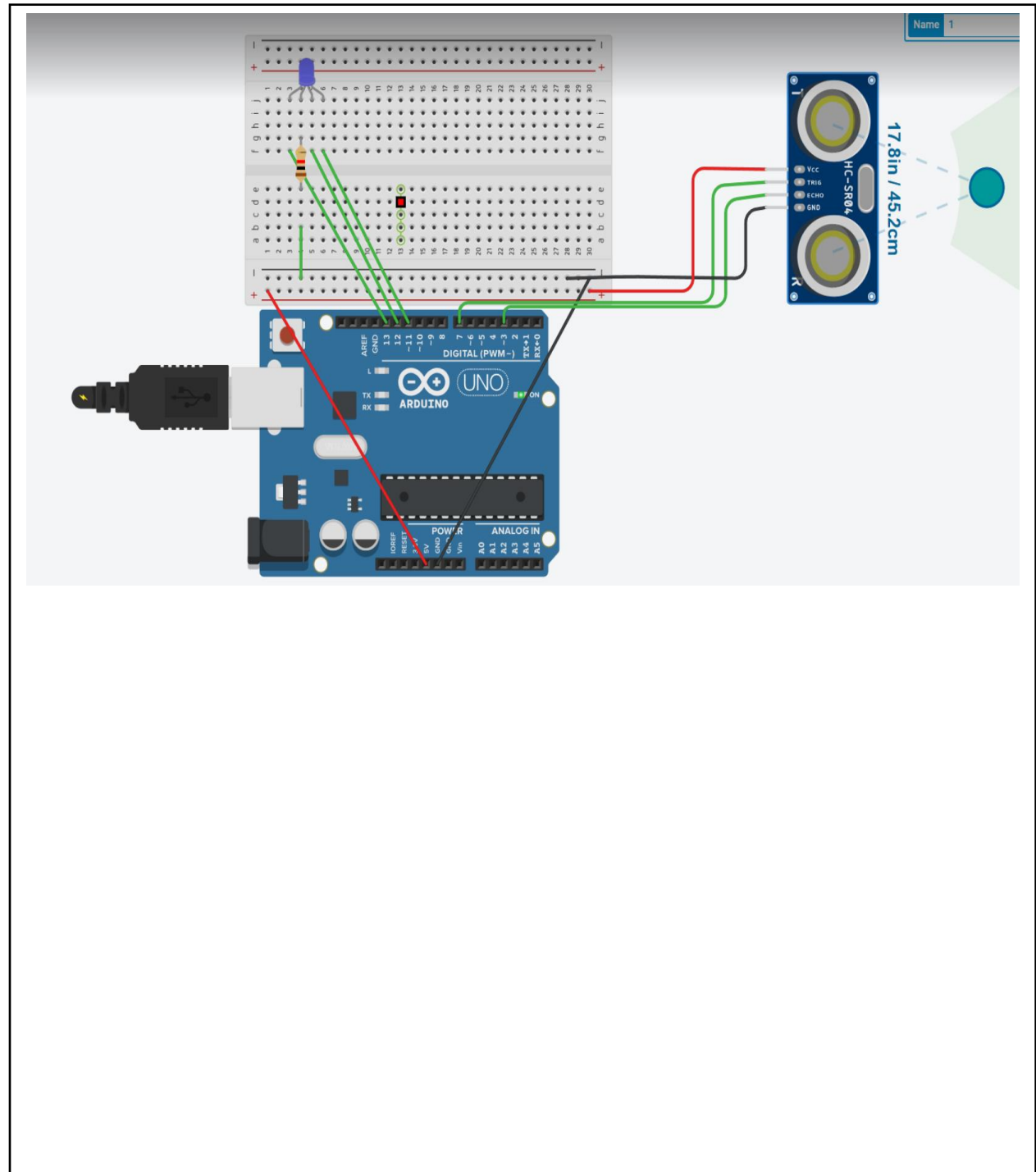Take a picture of your distance sensor and include it here, please reduce the size and quality as it will be too large else 😊



## Activity 5.3: 1602 LCD Display

Fritzing

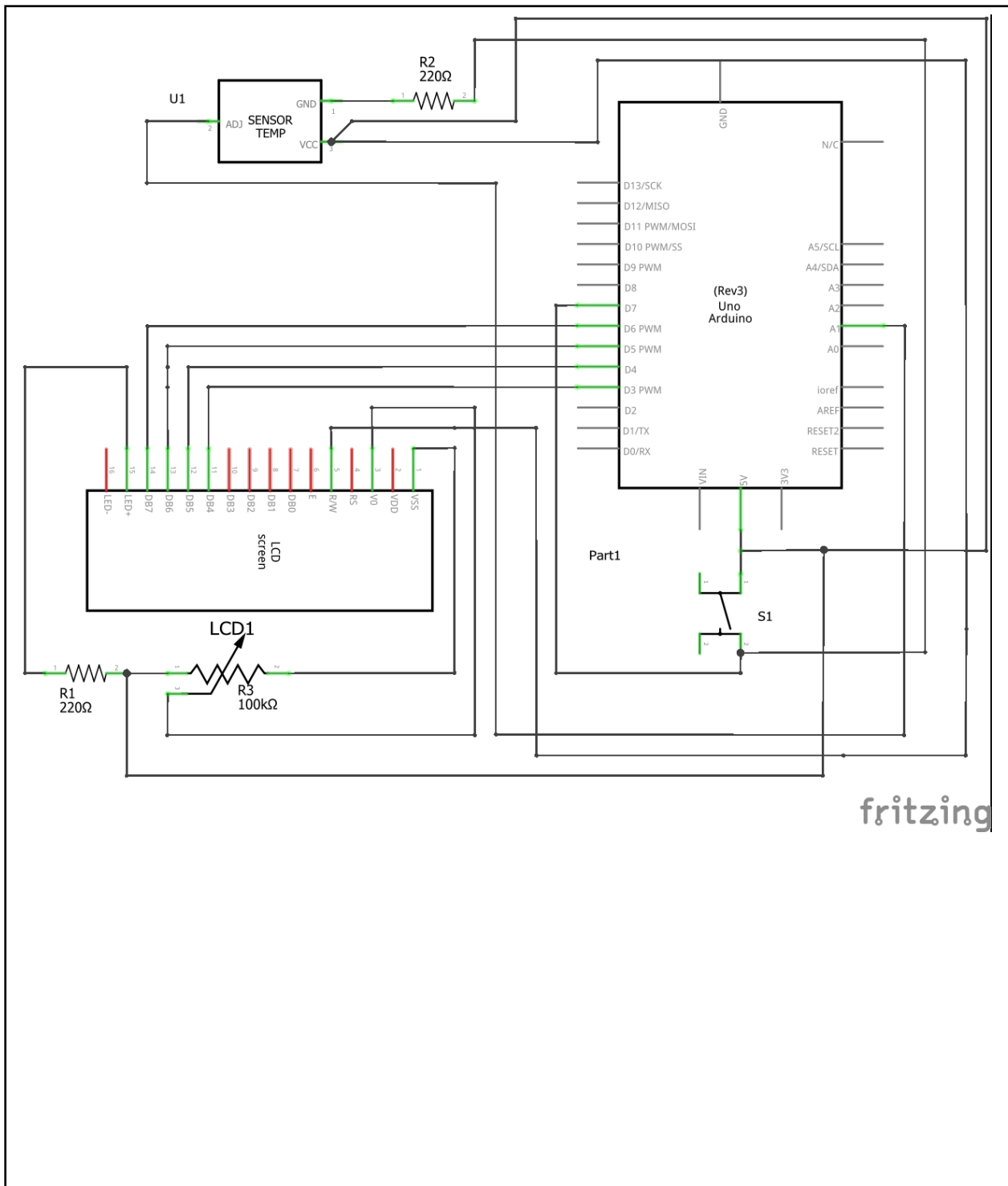

## Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486



LiquidCrystal lcd(12, 11, 5, 4, 3, 2);
int switchInput=13;

void setup() {
  // Set the number of columns and rows on the LCD:
  lcd.begin(16, 2);
  Serial.begin(9600);
}

//Loop Method()
void loop()
{
  int analogReading = analogRead(A0);
  float degreeC = analogReading*500.0/1024.0;
  float degreeF = (degreeC*9.0/5.0)+32;
  int switchState = digitalRead(switchInput);
  Serial.println(switchState);

  //Using if and else condition:
  if (switchState == LOW)
  {
    lcd.print(degreeC);
    lcd.print(" C");
    lcd.setCursor(9,0);
    lcd.print("US_2021");
    delay(1000);
    lcd.clear();
  }
  else
  {
    lcd.print(degreeF);
    lcd.print(" F");
    lcd.setCursor(9,0);
    lcd.print("US_2021");
    delay(1000);
    lcd.clear();
  }
}
```

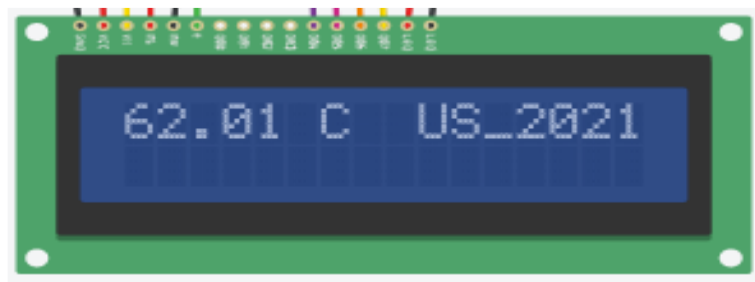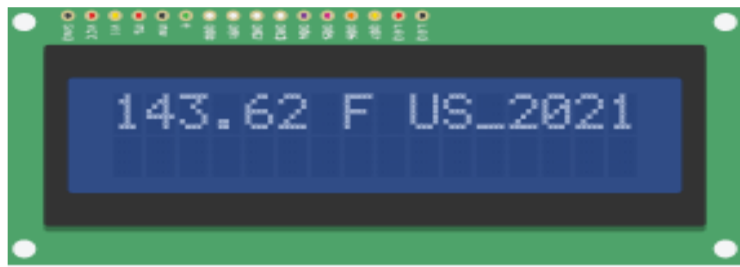
Take a picture of your LCD and include it here, please reduce the size and quality as it will be too large else 😊



## Workbook 6

### Activity 6.1: PWM

Fritzing

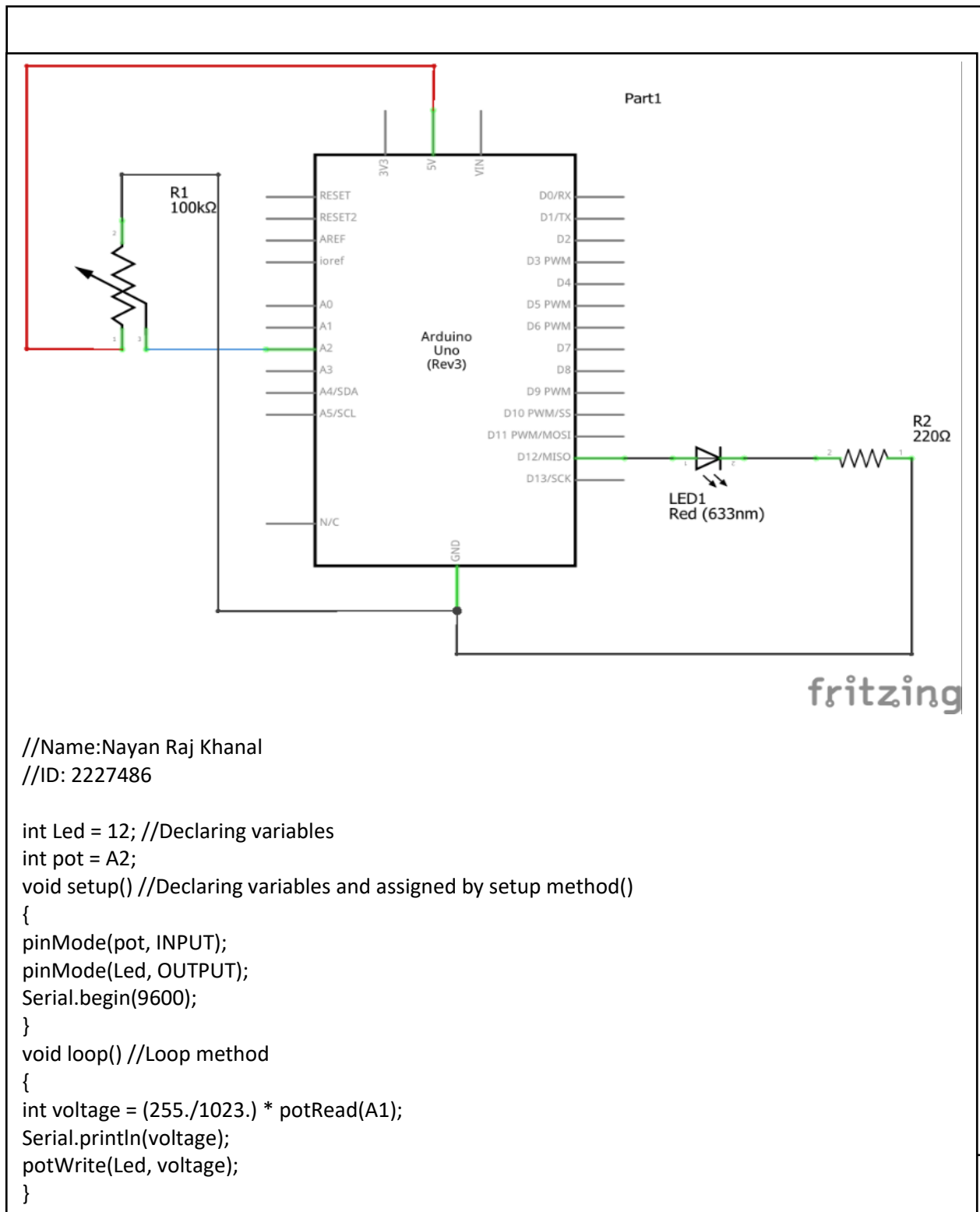





```
//Name:Nayan Raj Khanal
```

```
//ID: 2227486
```

```
// include the library code:
```

```
#include <LiquidCrystal.h>
```

```
char test[10];// input the value
```

```
LiquidCrystal lcd(12, 11, 5, 4, 3, 2);//// initialize the library with the numbers of the interface pins
```

```
void setup() { // starting the program
```

```
lcd.begin(16, 2); // lcd communication begin
```

```
Serial.begin(9600); // serial communication begin
```

```
}
```

```
void loop() {
```

```
Serial.readBytes(test,6);
```

```
lcd.print(test); // print the value i lcd
```

```
delay(50); // wait for 50 millisecond
```

```
lcd.clear(); // clear the lcd
```

```
}
```

```
Arduino 2:
```

```
char a[10]; // input of value
```

```
void setup() { // starting the program
```

```
Serial.begin(9600); // serial communication begin
```

```
}
```

```
void loop() { // starting the loop
```

```
while(Serial.available()>0){
```

```
int i = 0;
```

```
char c = Serial.read(); // value input is equal to value in cd
```

```
if(c!='\n'){
```

```
a[i]=c;
```

```
i++;
```

```
}
```


```
Serial.write(a, 1);
```

```
}
```

```
}
```

## Activity 7.2: 2 Arduinos – using Serial I/O

Fritzing

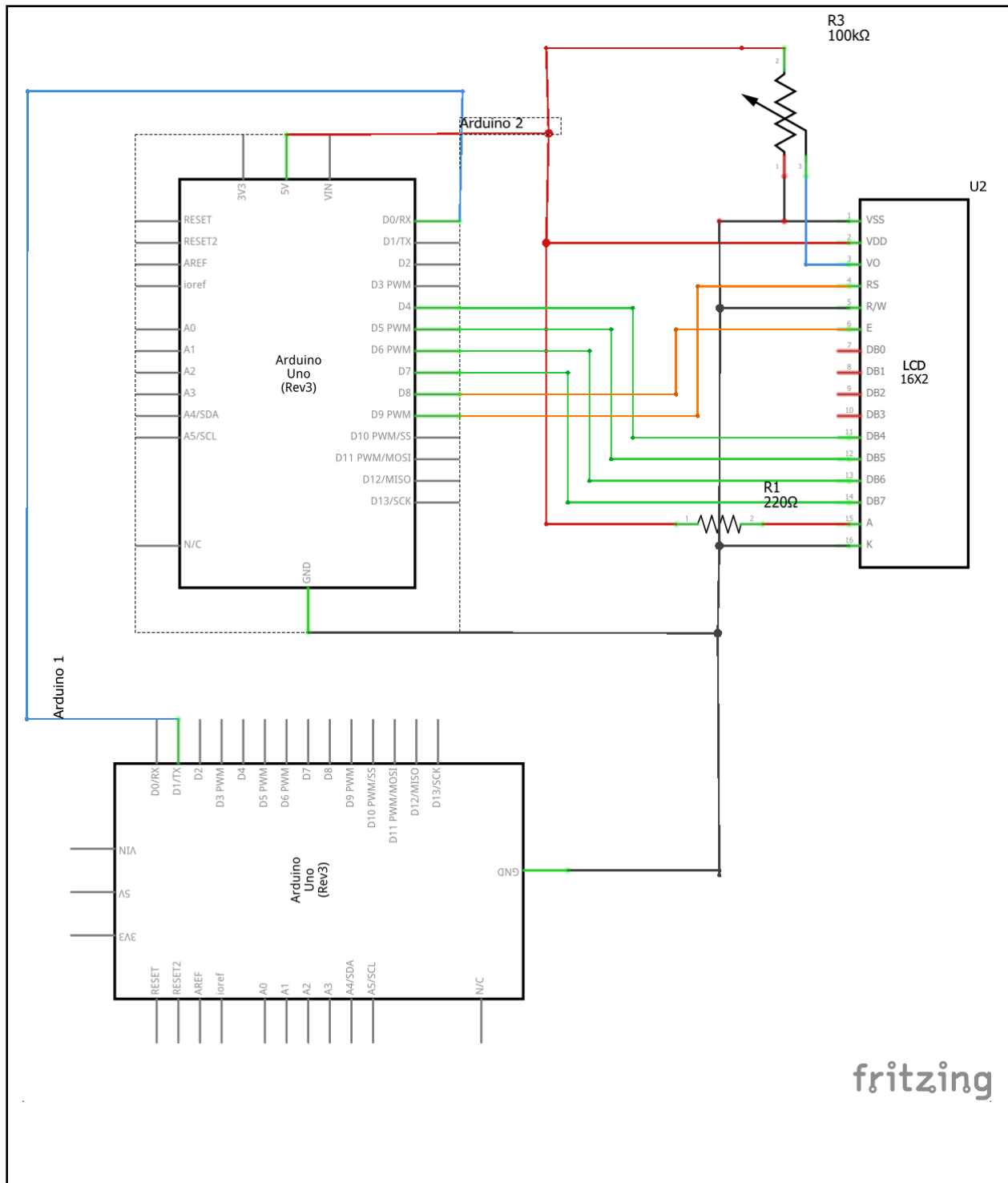

## Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486

// include the library code:
#include <LiquidCrystal.h>

char test[10]; // input the value

LiquidCrystal lcd(12, 11, 5, 4, 3, 2); // initialize the library with the numbers of the interface pins

void setup() { // starting the program
  lcd.begin(16, 2); // lcd communication begin
  Serial.begin(9600); // serial communication begin
}

void loop() {
  Serial.readBytes(test, 6);
  lcd.print(test); // print the value i lcd
  delay(50); // wait for 50 millisecond
  lcd.clear(); // clear the lcd
}

Arduino 2:


// student name: Kaushal Rai
// Student ID: 2226684
char name[10] = "Kaushal" ;

void setup() {
  Serial.begin(9600);
}

void loop() {
  Serial.write(name, 6);
  delay(100);
}
```

## Workbook 8
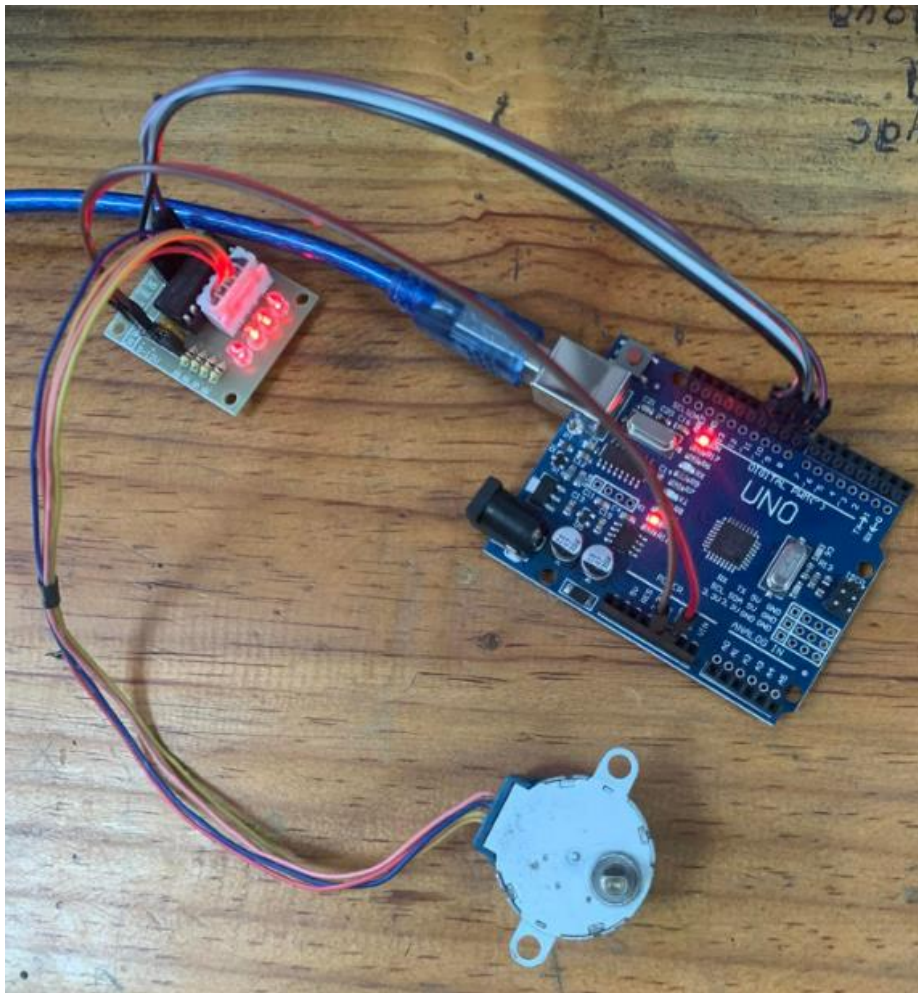
### Activity 8.1: Stepper Motor Circuit Diagram



Circuit Diagram

## Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486

#include <AccelStepper.h>

#define HALFSTEP 8

// Motor pin definitions
#define motorPin1 8 // IN1 on the ULN2003 driver 1
#define motorPin2 9 // IN2 on the ULN2003 driver 1
#define motorPin3 10 // IN3 on the ULN2003 driver 1
#define motorPin4 11 // IN4 on the ULN2003 driver 1

// Initialize with pin sequence IN1-IN3-IN2-IN4 for using the AccelStepper with 28BYJ-48
AccelStepper stepper1(HALFSTEP, motorPin1, motorPin3, motorPin2, motorPin4);

void setup() {
  stepper1.setMaxSpeed(2000.0);
  stepper1.setAcceleration(1000.0);
  stepper1.setSpeed(2000);
  stepper1.moveTo(2000);
} //--(end setup)---

void loop() {

  //Change direction when the stepper reaches the target position
  if (stepper1.distanceToGo() == 0) {
    stepper1.moveTo(-stepper1.currentPosition());
  }
  stepper1.run();
}
```

## Activity 8.2: 2 Stepper Motors

### Arduino Program

```
//Name:Nayan Raj Khanal
//ID: 2227486

#include <Stepper.h>
#include <AccelStepper.h>
#define HALFSTEP 8
int Pin1 = 8;//IN1 is connected to 8
int Pin2 = 9;//IN2 is connected to 9
int Pin3 = 10;//IN3 is connected to 10
int Pin4 = 11;//IN4 is connected to 11
int switchCW =2;
int switchCCW =3;
int pole1[] ={0,0,0,0, 0,1,1,1, 0};
int pole2[] ={0,0,0,1, 1,1,0,0, 0};
int pole3[] ={0,1,1,1, 0,0,0,0, 0};
int pole4[] ={1,1,0,0, 0,0,0,1, 0};
int poleStep = 0;
int dirStatus = 3;

void setup()
{
  pinMode(Pin1, OUTPUT);//define pin for in1
  pinMode(Pin2, OUTPUT);//define pin for in2
  pinMode(Pin3, OUTPUT);//define pin for in3
  pinMode(Pin4, OUTPUT);//define pin for in4

  pinMode(switchCW,INPUT_PULLUP);// CW (Clock Wise)push button pin as input
  pinMode(switchCCW,INPUT_PULLUP);//CCW(Anti ClockWise) push button pin as input
}
```

```

void loop(){
  if(digitalRead(switchCCW) == LOW) {
    dirStatus =1;
  }else if(digitalRead(switchCW) == LOW) {
    dirStatus = 2;
  }
  if(dirStatus ==1){
    poleStep++;
    driveStepper(poleStep);
  }else if(dirStatus ==2){
    poleStep--;
    driveStepper(poleStep);
  }else{
    driveStepper(8);
  }
  if(poleStep>7){
    poleStep=0;
  }
  if(poleStep<0){
    poleStep=7;
  }
  delay(1);
}

void driveStepper(int c)
{
  digitalWrite(Pin1, pole1[c]);
  digitalWrite(Pin2, pole2[c]);
  digitalWrite(Pin3, pole3[c]);
  digitalWrite(Pin4, pole4[c]);
}

```



## Workbook 9

### Activity 9.1: Windscreen Wiper Code using Servos & Temperature Sensor

```
//Name:Nayan Raj Khanal
//ID: 2227486

#include<Servo.h> //importing library
//creating object for two servo to control
Servo servo1;
Servo servo2;
int pos=0; //initial position value 0 for servo

void setup ()
{
servo1.attach(6); //servo1 connected to 6 no. digital pin
servo2.attach(9); //servo2 connected to 9 no. digital pin
  Serial.begin(9600); //Serial monitor enabled
}
void loop()
{
int sensor=analogRead(A0); //variable for reading Analog data of temperature sensor
float cel=sensor*500/1023.0; //calculating temperature using formula
Serial.println(cel); //printing output in serial monitor
if (cel>=20){ //if condition satisfied, codes in block below runs
  for(pos=0;pos<180;pos++)
  { //rotates both servo at 180 degree from 0
    servo1.write(pos);
    servo2.write(pos);
    delay(30); }
```

```
for(pos=180;pos>0;pos--)
{ //rotates both servo at 0 degree from 180
  servo1.write(pos);
  servo2.write(pos);
  delay(30);
}
}
else{ //condition not satisfied servo stays at initial position
  servo1.write(pos);
  servo2.write(pos);
  delay(50);
}
}
```

## Individual Project (50%)

### Rationale

Throughout the module you have used a range of sensors and actuators with an Arduino to complete weekly tasks. For the mini project we would like you to research and create a small embedded project in an area of your choice, such as:

- Games
- Networking
- IT Security
- Systems Engineering
- Smart Technology
- Artificial Intelligence

Previous projects have included a reaction game that gives a score depending on how fast you hit a button, this has buttons to restart the application, and an LCD to show scores, and information.

This project should be your own work, **YOU MUST NOT COPY A PROJECT FROM THE INTERNET.**

### Timescales

This project should be started around week 5 and continue until the deadline, when it will be submitted in the Portfolio.

### Equipment

You are free to use Tinkercad, or your own kit.

### The Project

#### Step 1 produce a detailed description of your project.

This should clearly describe what you are intending to build and may contain some diagrams of how the sensor/switches input is to be processed by the Arduino. Then what kind of output is intended to be seen or heard by the user. Please mention any tools you intend to use.

#### Step 2 Circuit Diagram & Fritzing Schematic

You are required to produce a circuit diagram of your work showing any calculations you made, so these might be suitable resistor values for any LED's you use. These calculations are covered on the module. The circuit diagram should not be hand drawn but should follow the format of circuits from the module.

### Step 3 A Program

You will need to write some software for this project and a listing of the code with suitable comments will need to be included.

### Step 4 Testing

You will be required to produce some suitable test data that you would expect to be able to measure such as voltages, test code.

Once your prototype is complete you will be expected to test your circuit and compare the actual values to your initial test data, and comment on the results.

### Step 5 Conclusions

You are required to write a summary of the work along with a short half page reflection on how you found the work.

### Layout

The report should be suitably laid out for a report, using headings, references if required in Harvard style, and appendices used for any lengthy code. All diagrams should be produced on a PC, and hand-written work is not acceptable.

### Marking

All sections carry equal marks.